

# What you are expected to know

- Ohm's Law
- Series & Parallel
- Kirchhoff's Rules
- Short circuits
- RC Circuit behaviour
- LEDs let current flow in only one direction


LED 

GND 

# Resistor Colour Code



Schematic Symbol

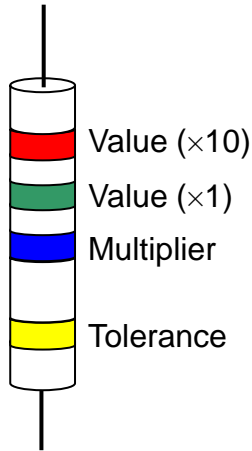


Colour	Value	Multiplier
Black	0	$10^0$
Brown	1	$10^1$
Red	2	$10^2$
Orange	3	$10^3$
Yellow	4	$10^4$
Green	5	$10^5$
Blue	6	$10^6$
Violet	7	$10^7$
Gray	8	$10^8$
White	9	$10^9$

Colour	Tolerance
Gold	5%
Silver	10%
None	20%


Hint – Use an ohmmeter!

# Electronics Circuit Diagrams

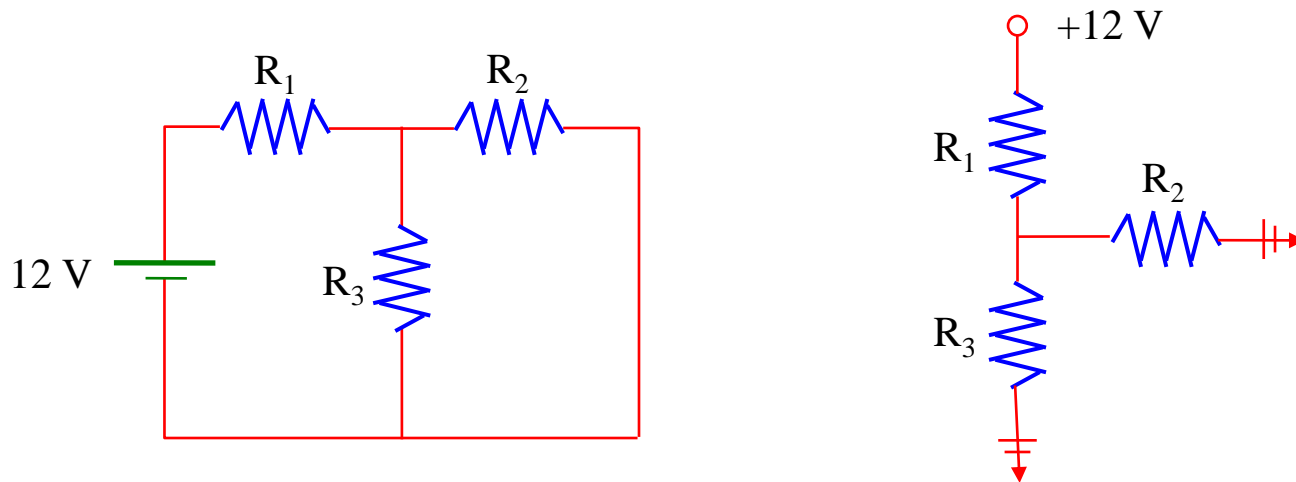


**Figure IV-8:** Standard and electronics style circuit diagrams.

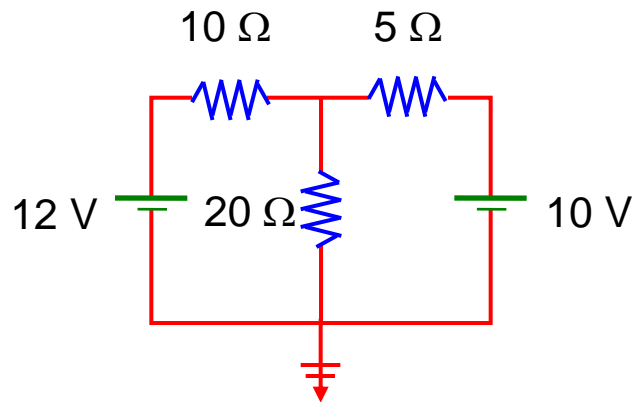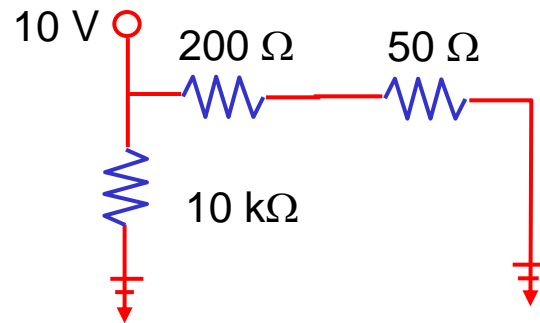
(a)




(c)




(b)

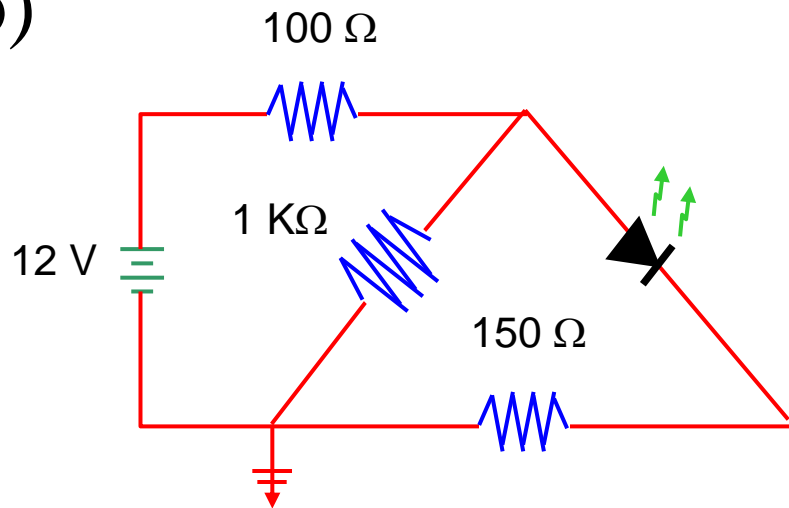

(d)

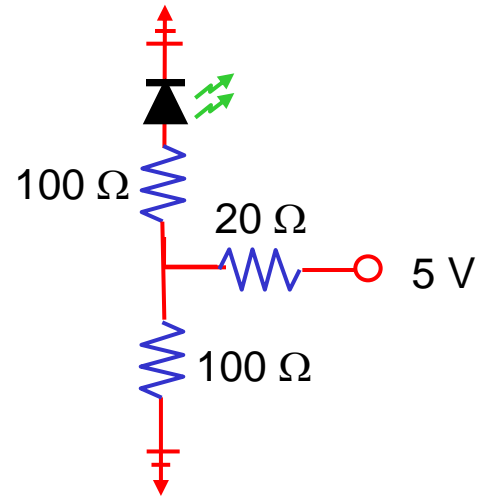


# Voltage Divider

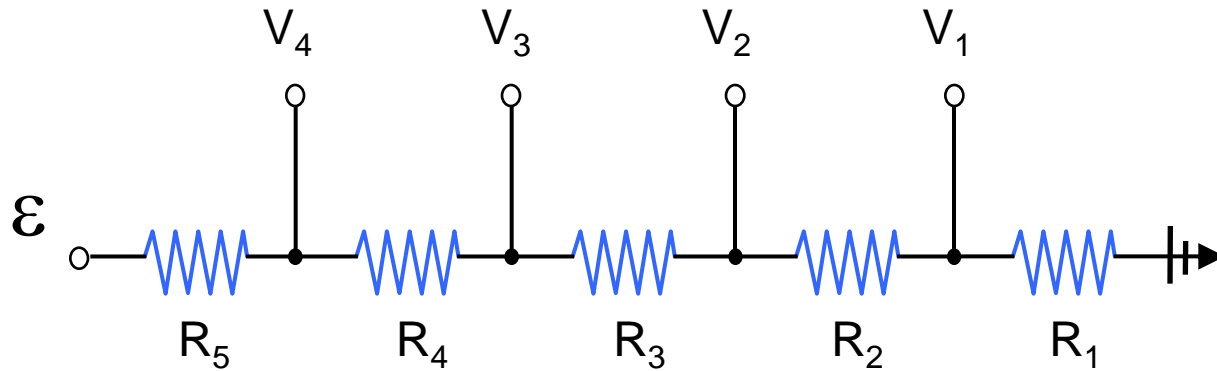


$$V_n = \frac{R_1 + \dots + R_n}{R_{Total}} \mathcal{E}$$

$V_n$  is voltage wrt ground

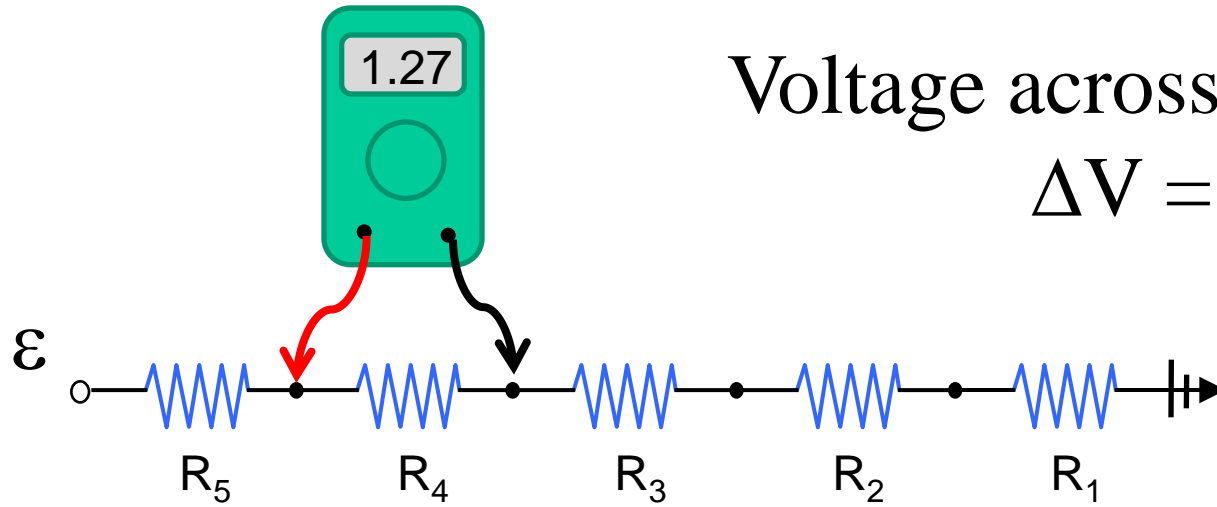

Voltage across = voltage drop

$$\Delta V = I \times R_4$$

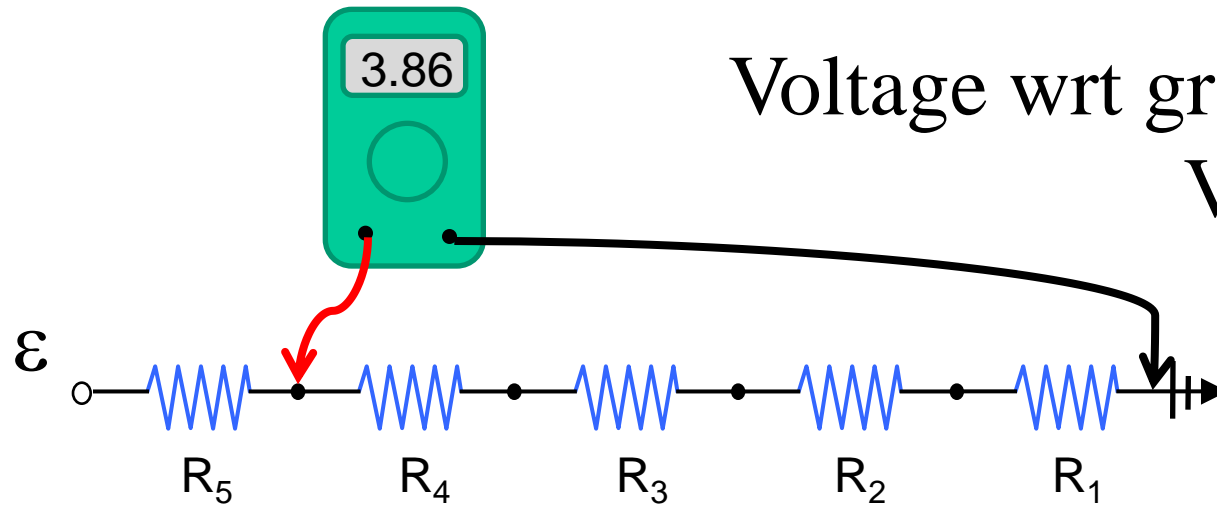


Voltage wrt ground = voltage

$$V_4$$
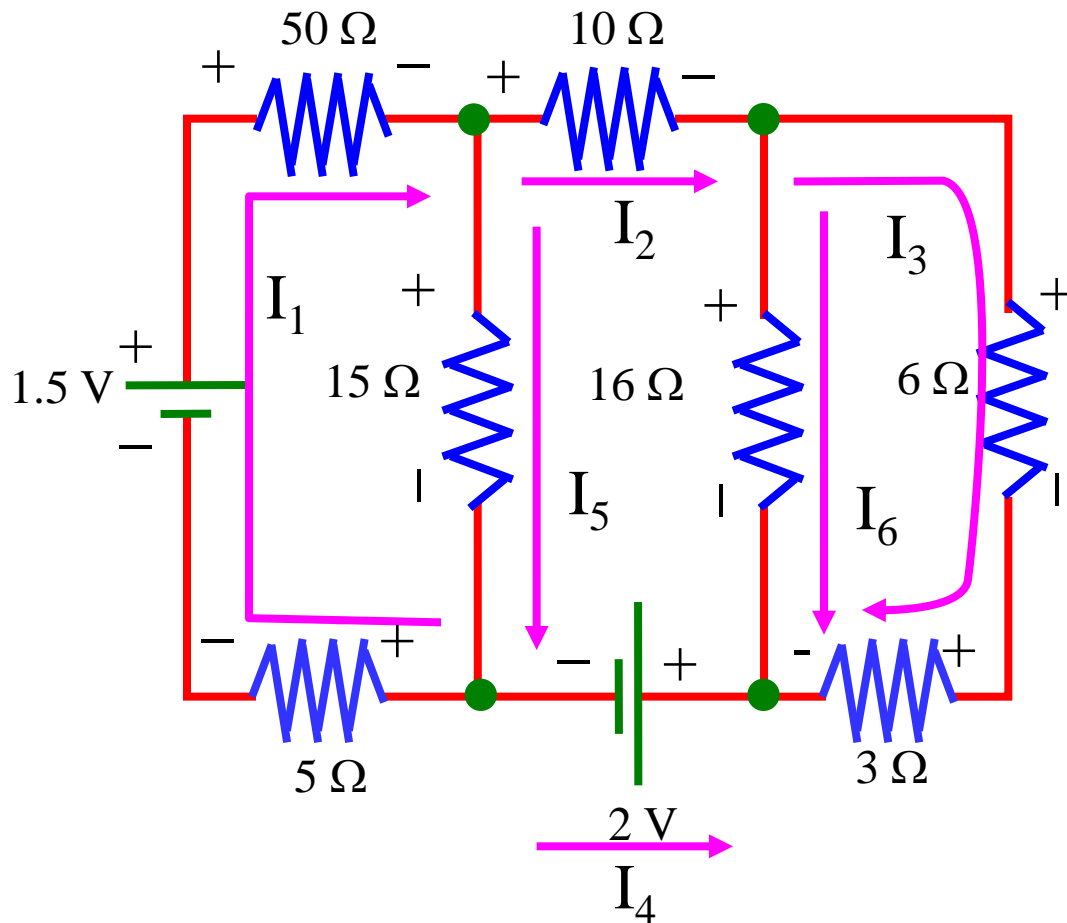
# Using Kirchhoff's Rules

- We use conventional (+) current
- Node/Junction: 3 or more wires join
- Branch: Path from one node to next
  - Assume one current and direction per branch
  - Current flows from high (+) to low (-)
  - $\Delta V = -IR$  if go in direction of current
  - $\Delta V = +IR$  if go opposite to current
- Sum of  $\Delta V$ 's around loop = 0 (KR1)
- Current Into node = current out (KR2)



$$1.5 - 50I_1 - 15I_5 - 5I_1 = 0$$

$$I_1 = I_2 + I_5$$


$$2 + 16I_6 + 10I_2 - 15I_5 = 0$$

$$I_2 = I_3 + I_6$$

$$-6I_3 - 3I_3 + 16I_6 = 0$$

$$I_6 + I_3 + I_4 = 0$$



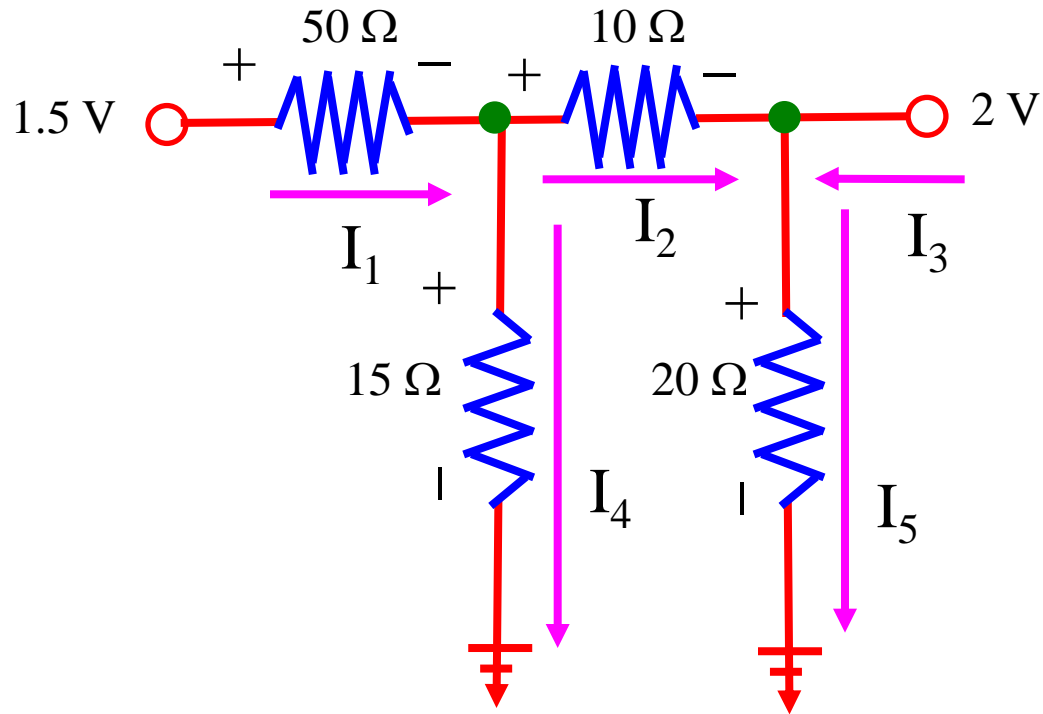

$$1.5 - 50I_1 - 15I_4 = 0$$


$$1.5 - 50I_1 - 10I_2 - 20I_5 = 0 \quad I_1 = I_2 + I_4$$

$$2 - 20I_5 = 0$$

$$I_5 = I_2 + I_3$$


$$2 + 10I_2 - 15I_5 = 0$$

# Short Circuit


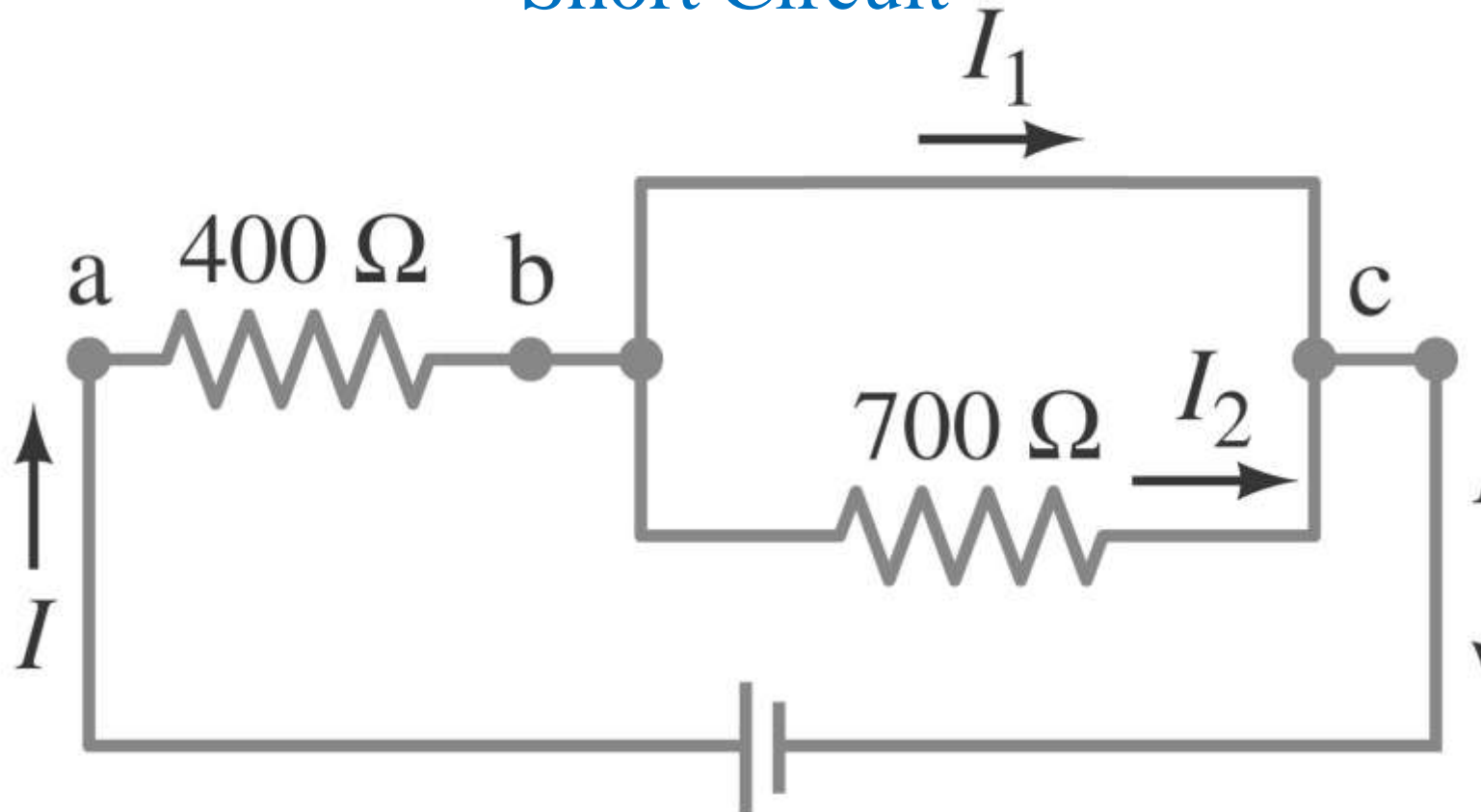



12.0 V


(a)

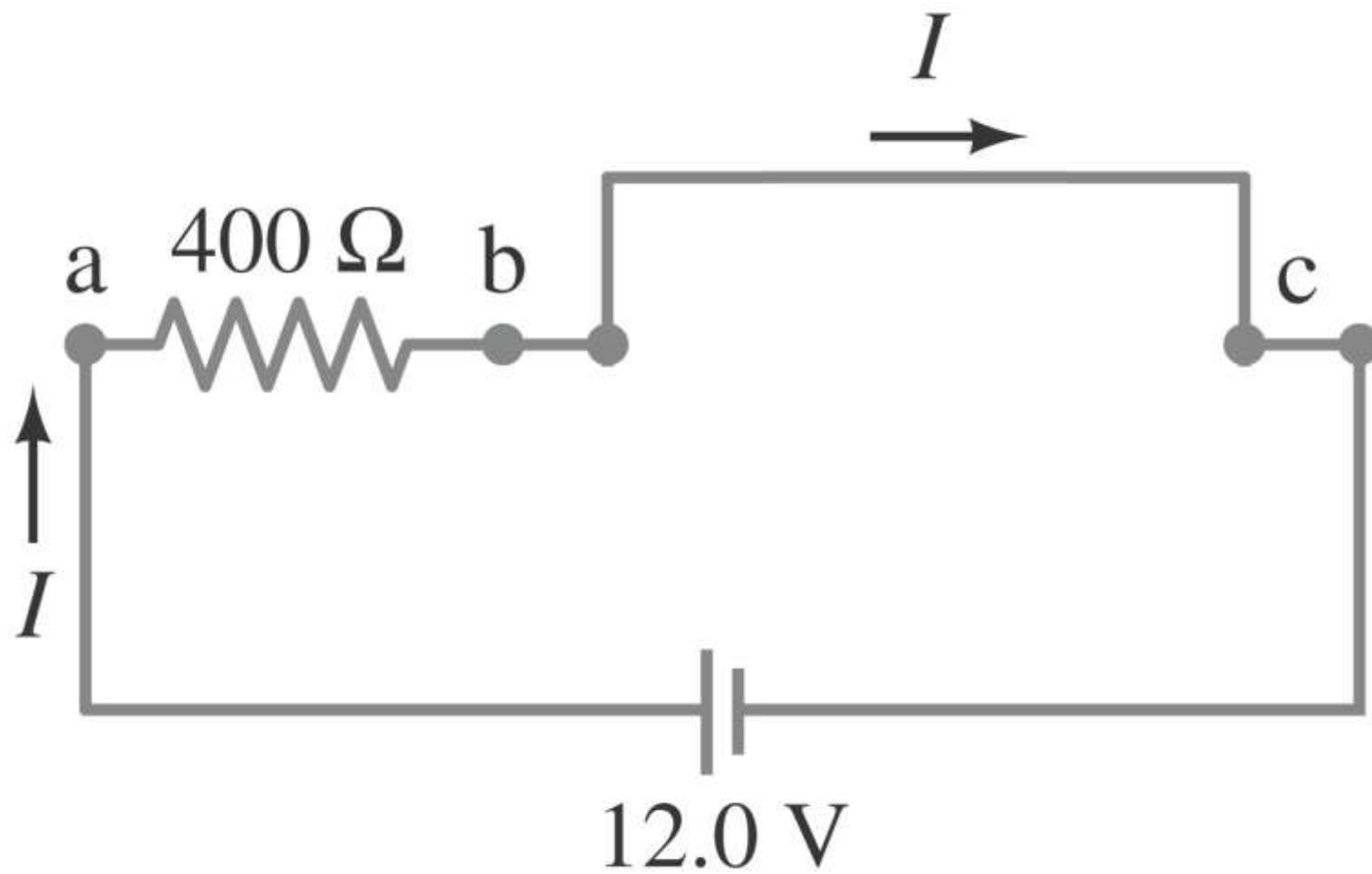

(a)

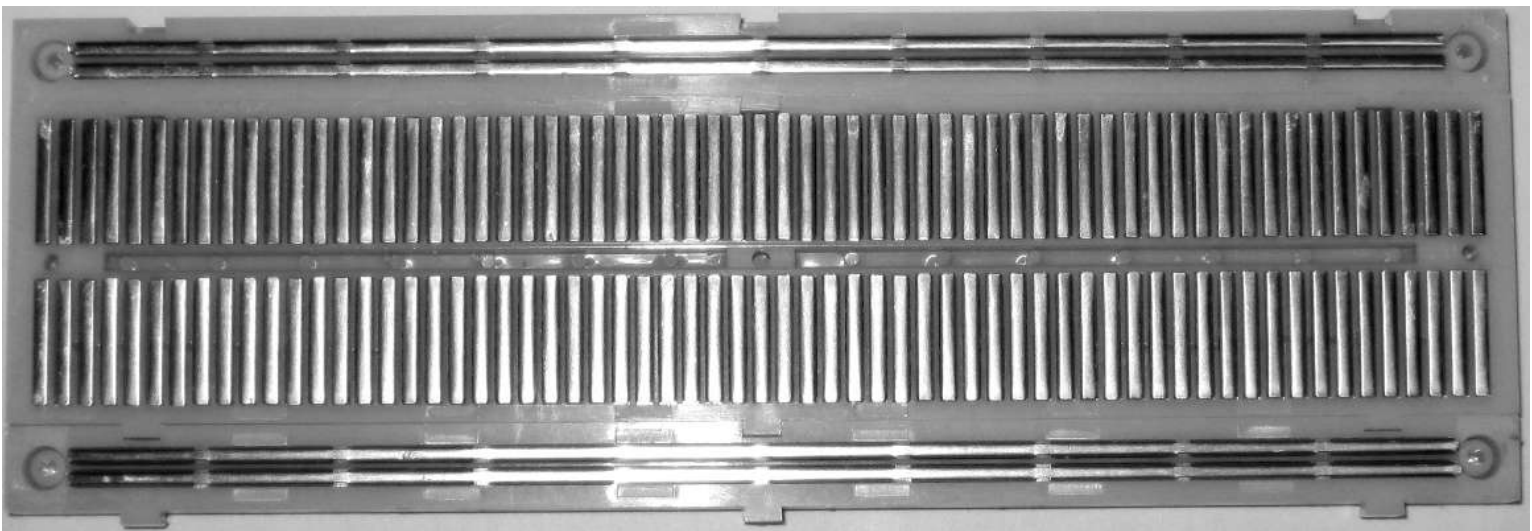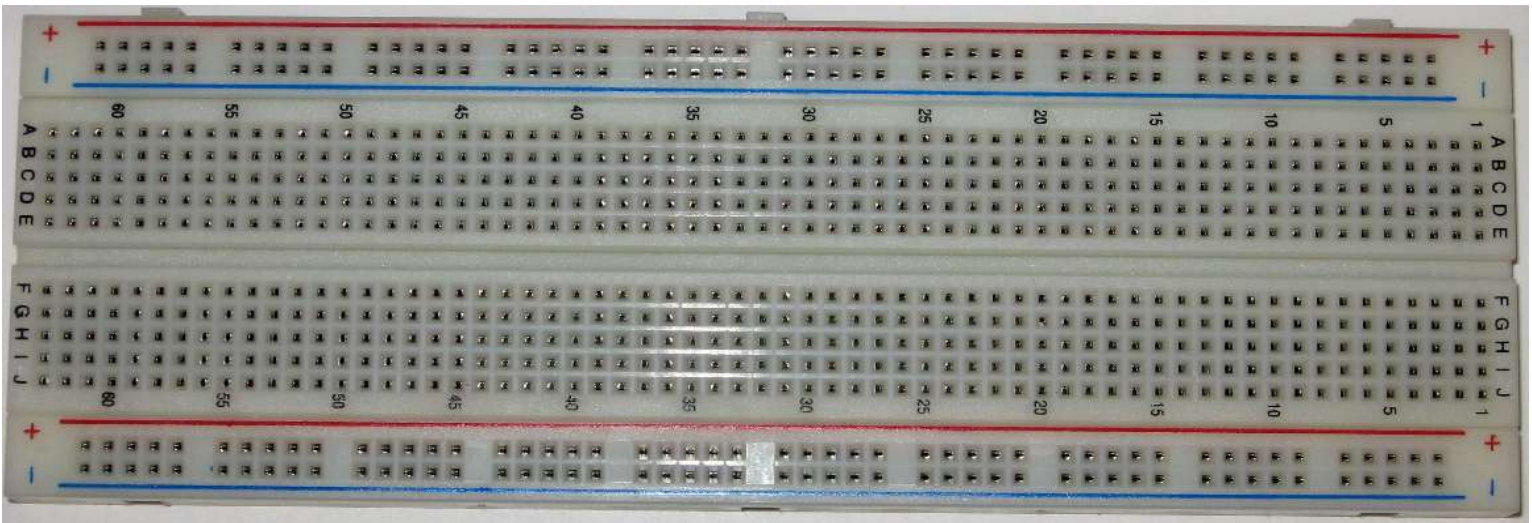

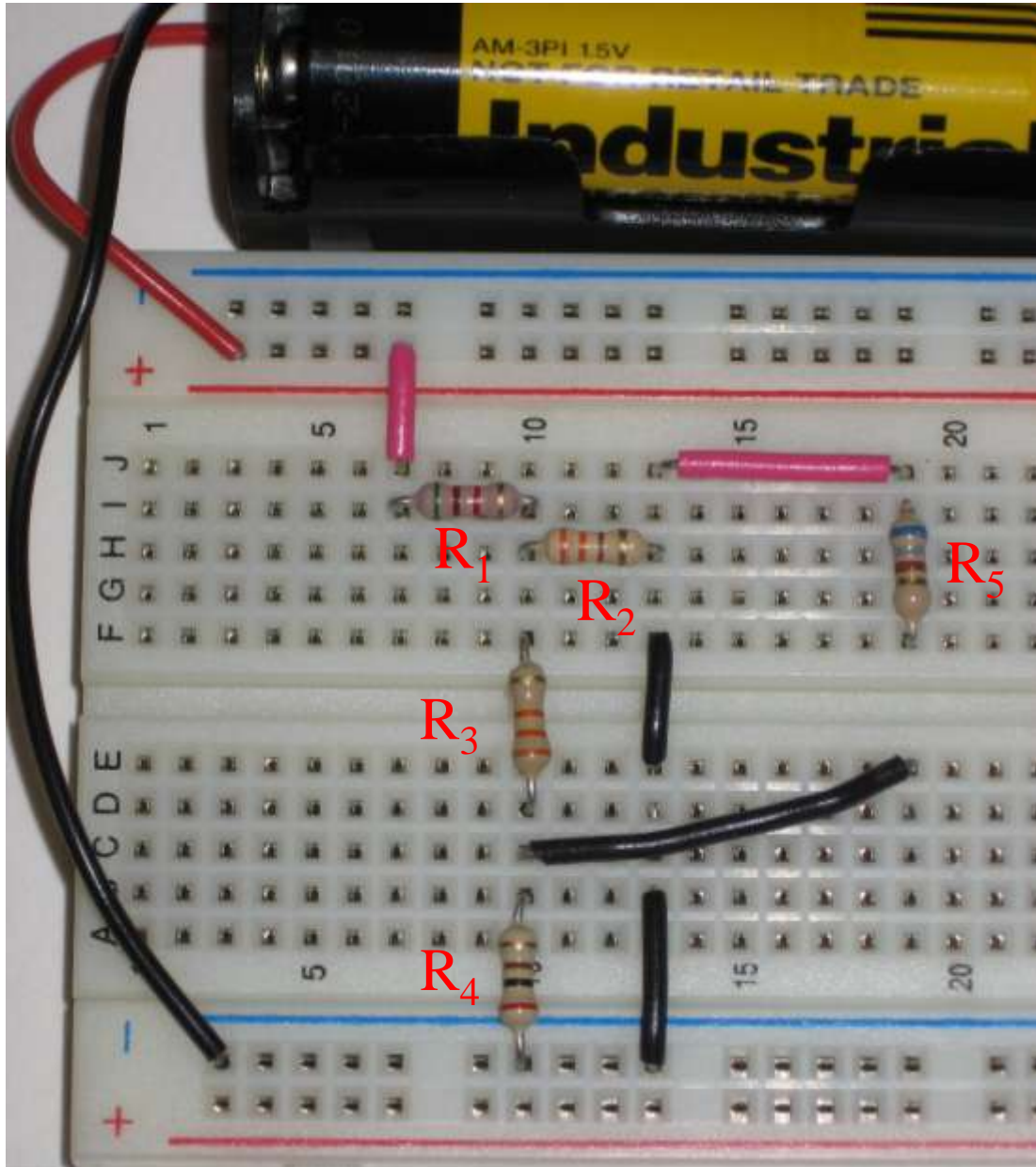


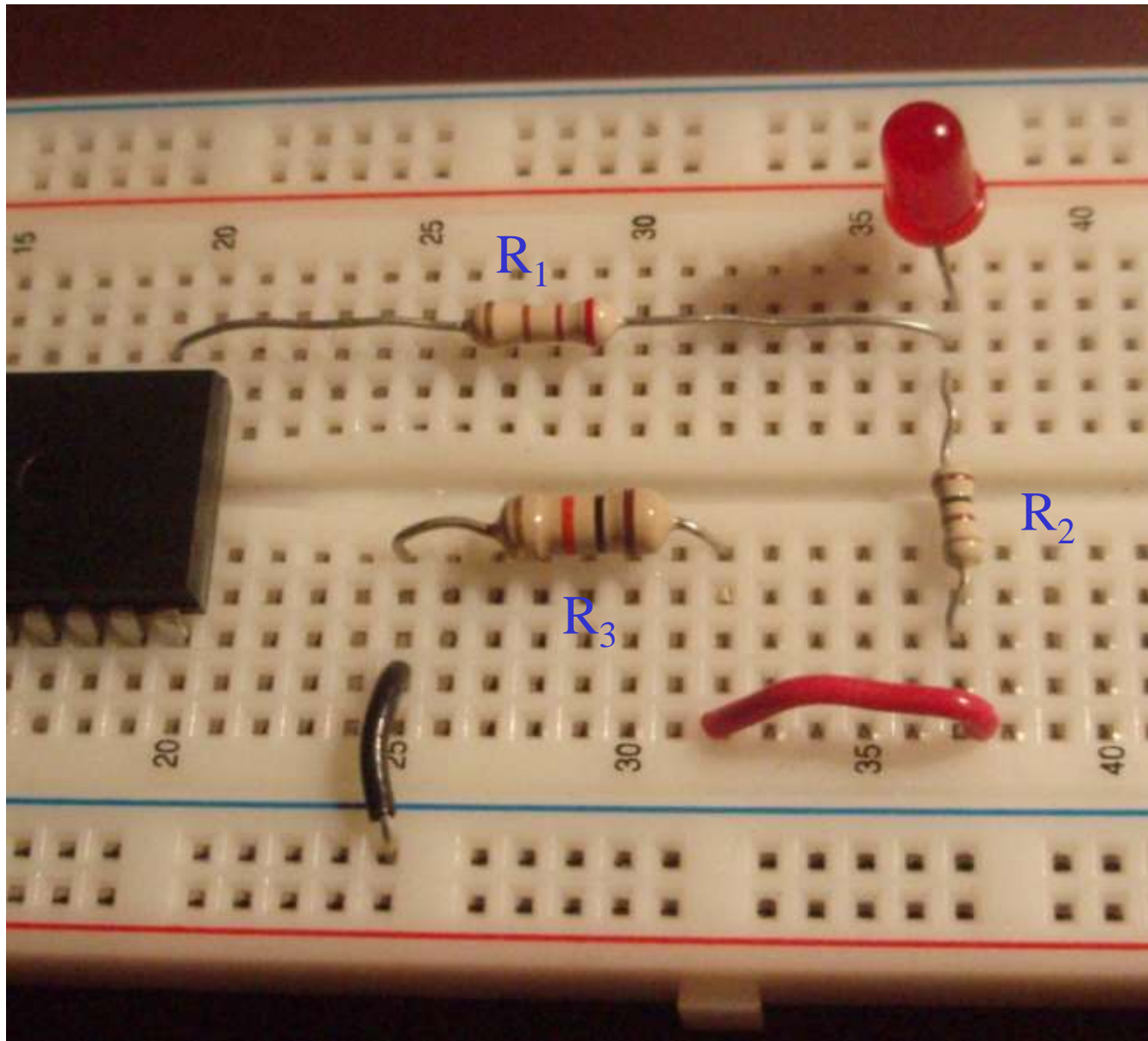

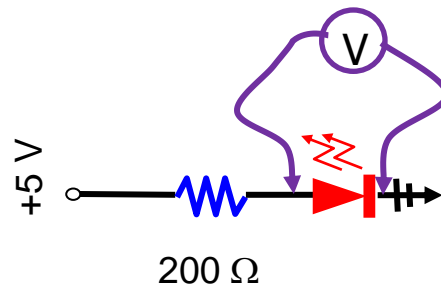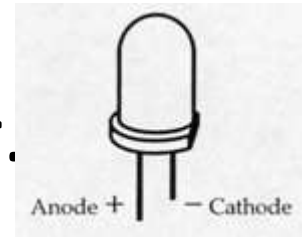
# LED

- Conventional current only flows one way




- Notch on cathode (-) end. Leg shorter.
- Operates at  $\sim 2$  Volts.




- Resistor controls current and brightness.

# LED Circuits

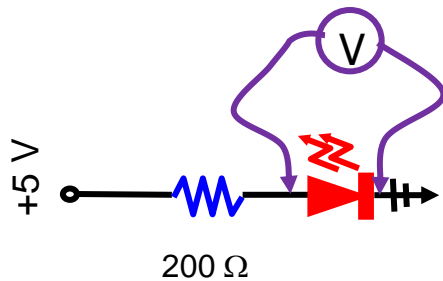


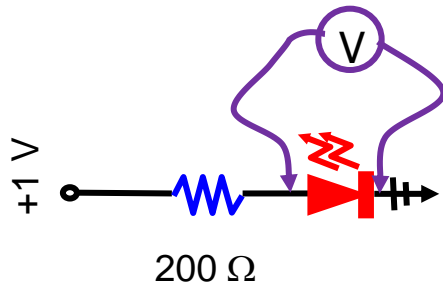- Assume Forward biased –  $V_F = 2\text{ V}$
- $5 = (200)I + 2$
- Since  $I > 0$ , assumption is true




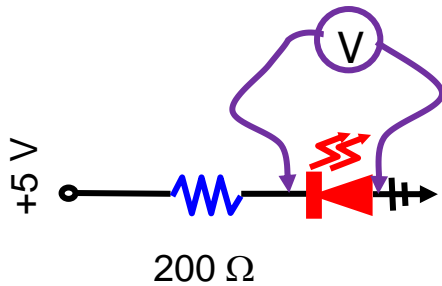- Assume Forward biased
- $1 = (200)I + 2$
- Since  $I < 0$ , assumption not true
- $I = 0$
- $1 = (200)(0) + V_{\text{LED}}$






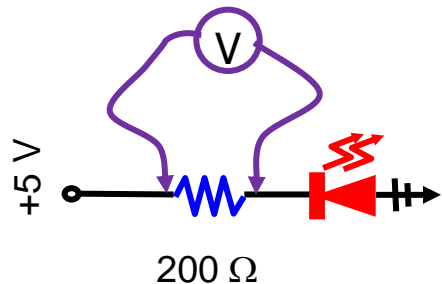Cannot use voltmeter across reverse-biased LED. The LED has a huge effective resistance. Voltmeters only accurate if  $R \ll R_{\text{voltmeter}}$ .



Workaround:
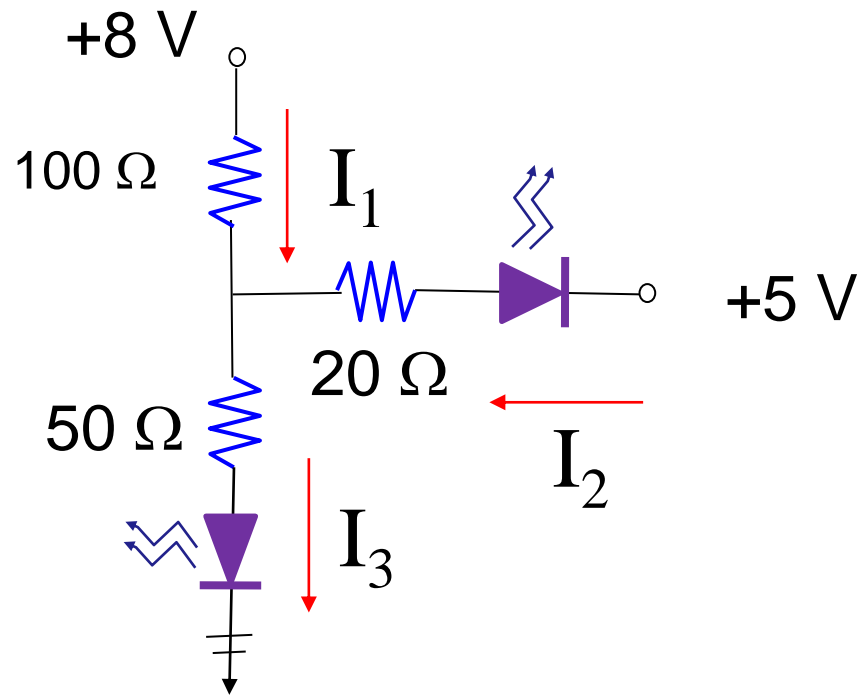
$$5 = \Delta V_{\text{resistor}} + \Delta V_{\text{LED}}$$




Assume current flow through LEDs correctly

$$I_1 + I_2 = I_3$$

$$8 \text{ V} = (100 \Omega)I_1 + (50 \Omega)I_3 + V_{\text{LEDB}}$$

$$5 \text{ V} = -V_{\text{LEDA}} + (20 \Omega)I_2 + (50 \Omega)I_3 + V_{\text{LEDB}}$$
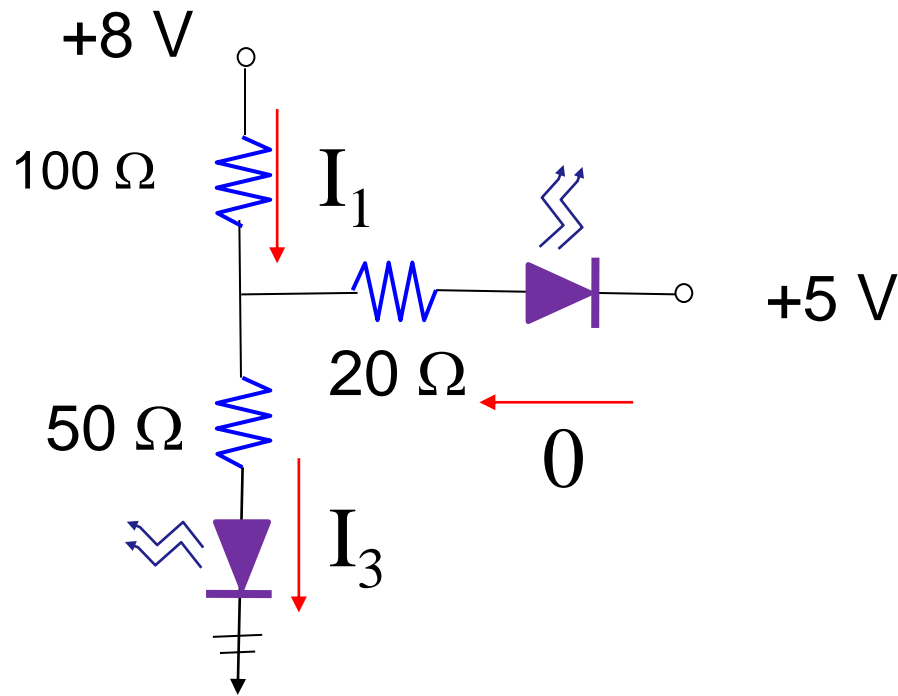
$$I_1 = 37/800 \text{ A}, I_2 = -3/160 \text{ A}, \text{ and } I_3 = 22/800 \text{ A}$$



Since current cannot be negative,  $I_2 = 0!$




$$I_1 + 0 = I_3$$

$$8 \text{ V} = (100 \text{ } \Omega)I_1 + (50 \text{ } \Omega)I_3 + V_{\text{LEDB}}$$

$$5 \text{ V} = -V_{\text{LEDA}} - (20 \text{ } \Omega)0 + (50 \text{ } \Omega)I_3 + V_{\text{LEDB}}$$

$$I_1 = I_3 = 6/150 \text{ A, and } V_{\text{LEDA}} = -1 \text{ V}$$
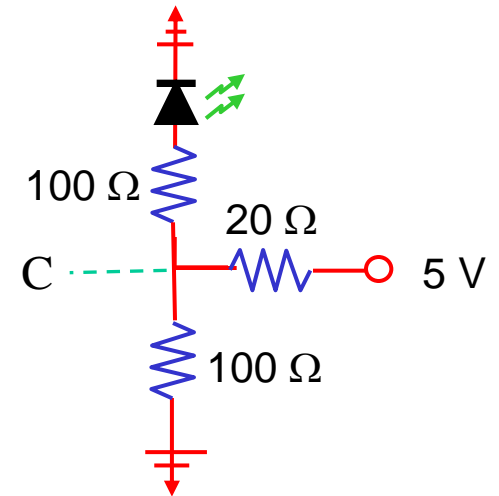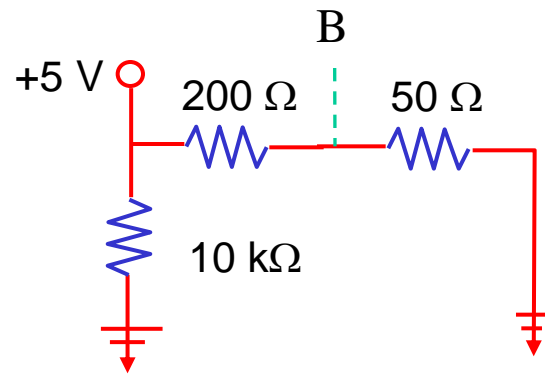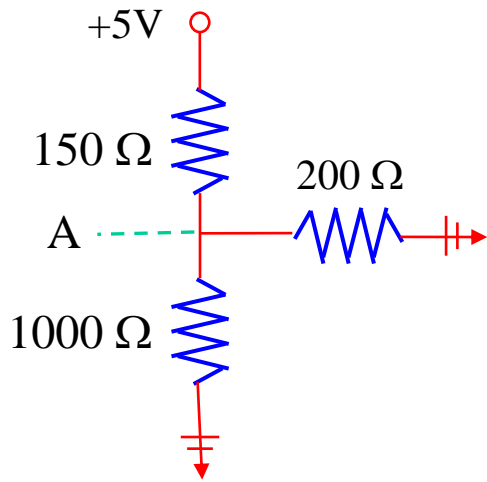
# Sketch what these circuits look like on a breadboard



What is the voltage wrt ground at the indicated points?