

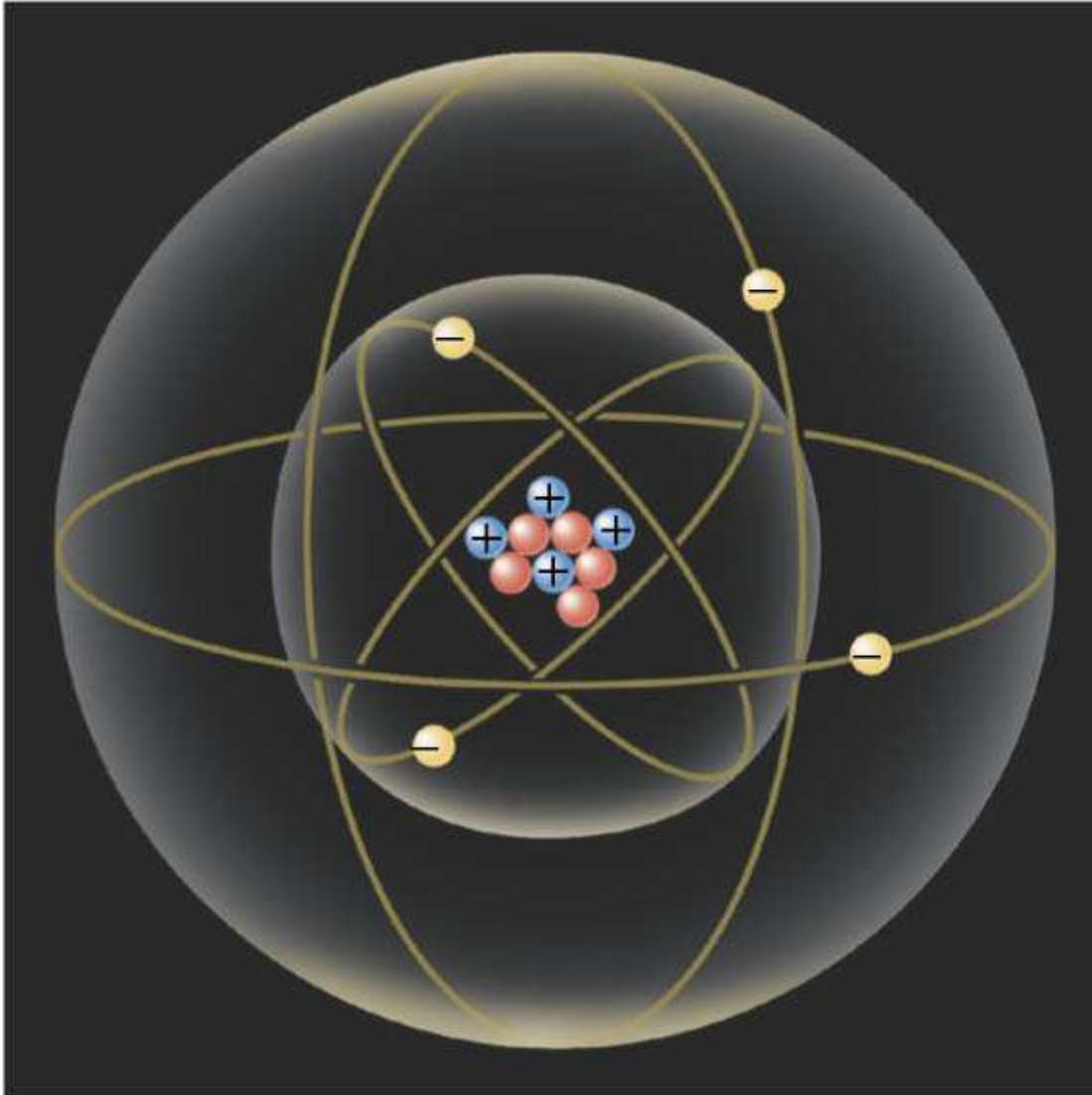



# Electric Charge, Energy, and Potential Difference

- − electron
- + proton
- neutron

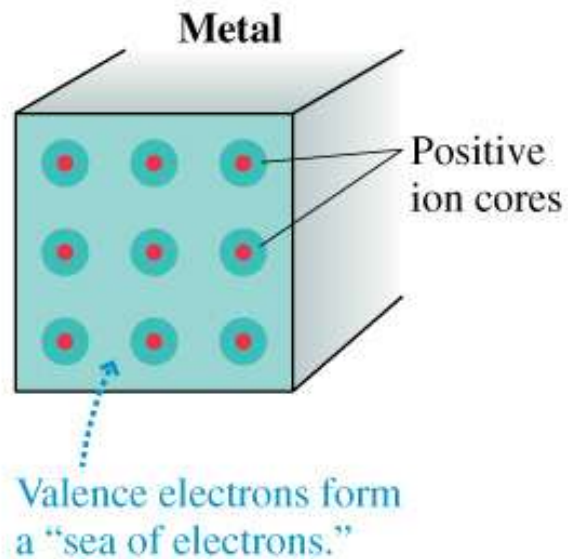


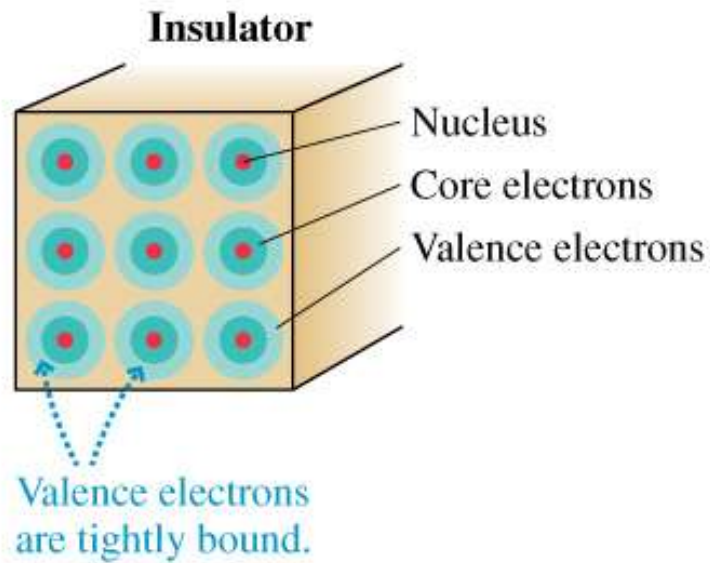Outer or “valence” electrons determine chemical and electrical properties of solids.




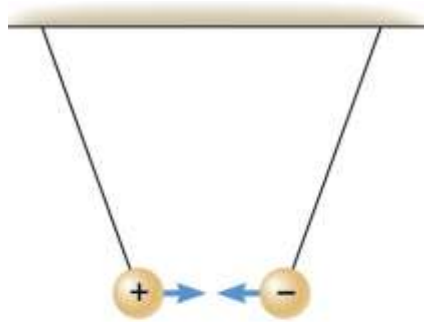


(a)

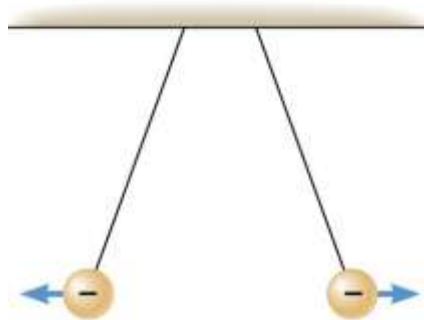



(b)

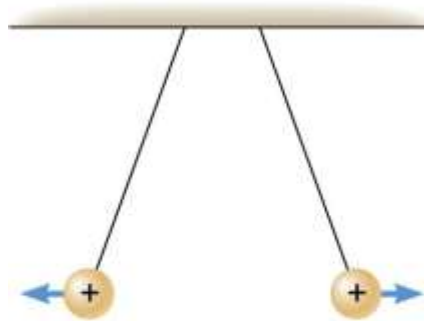


(c)

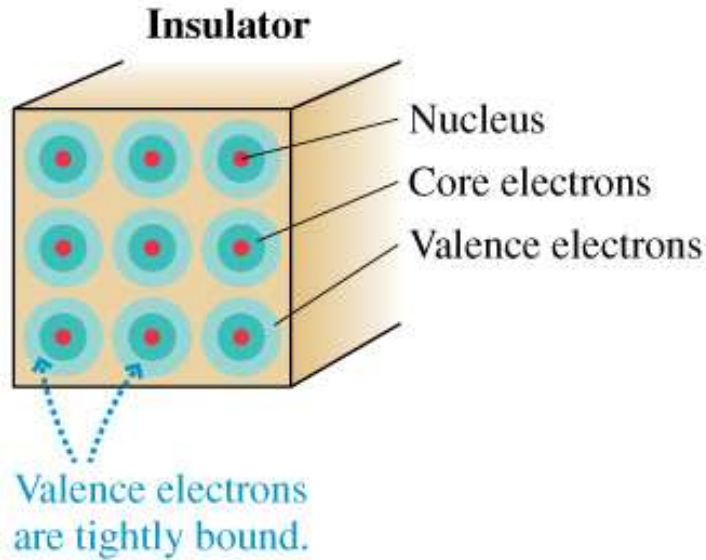

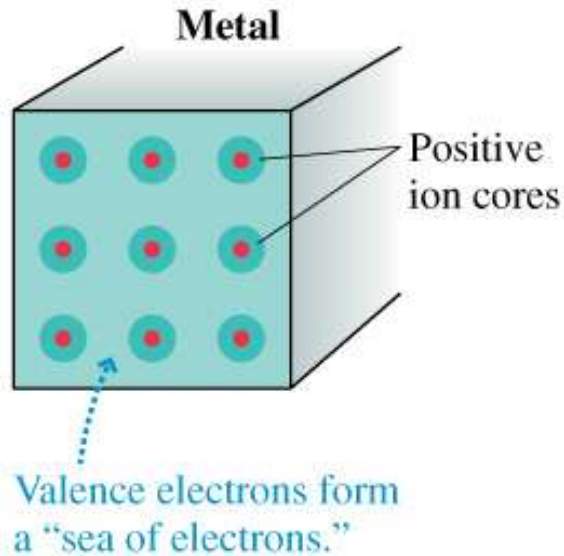 
Add charge to an insulator and it stays where it is put.



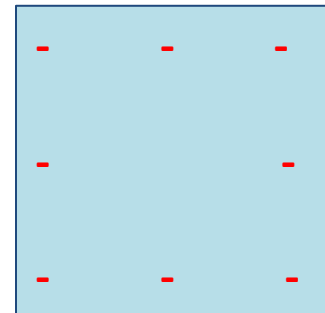
Add charge to a conductor and it spreads out.



F

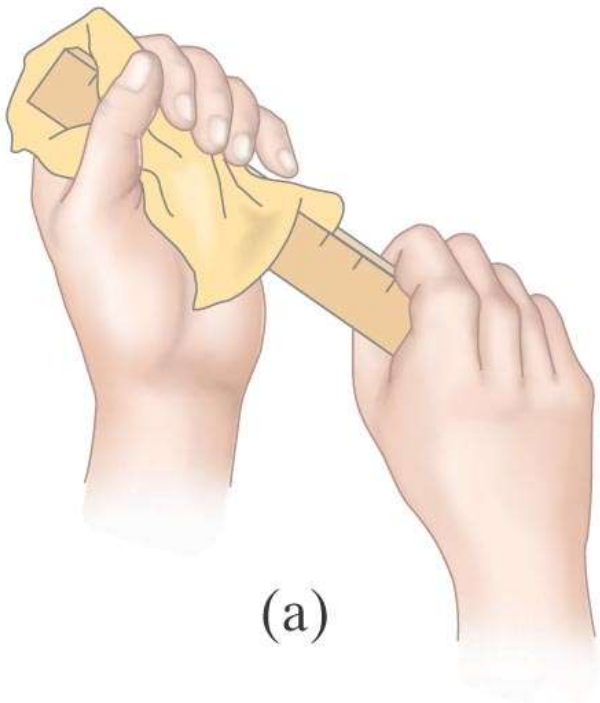

(a)

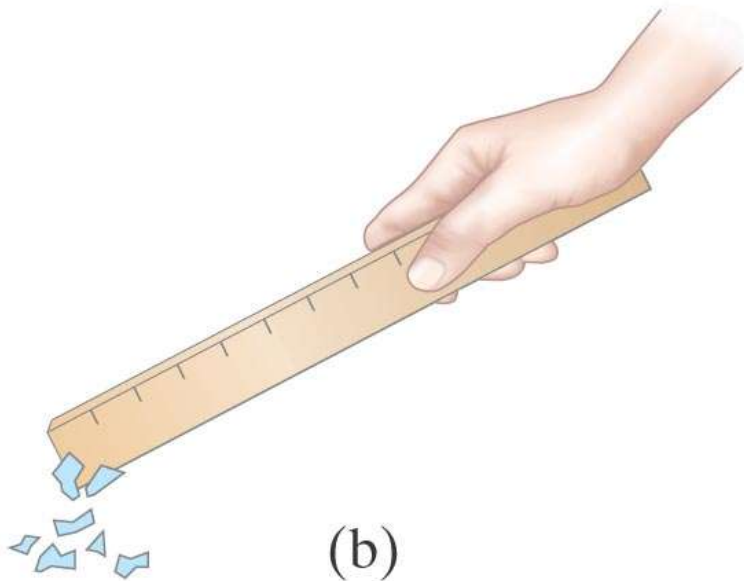


(b)



Copyright © 2008 Pearson Education, Inc.



(a) Neutral metal rod


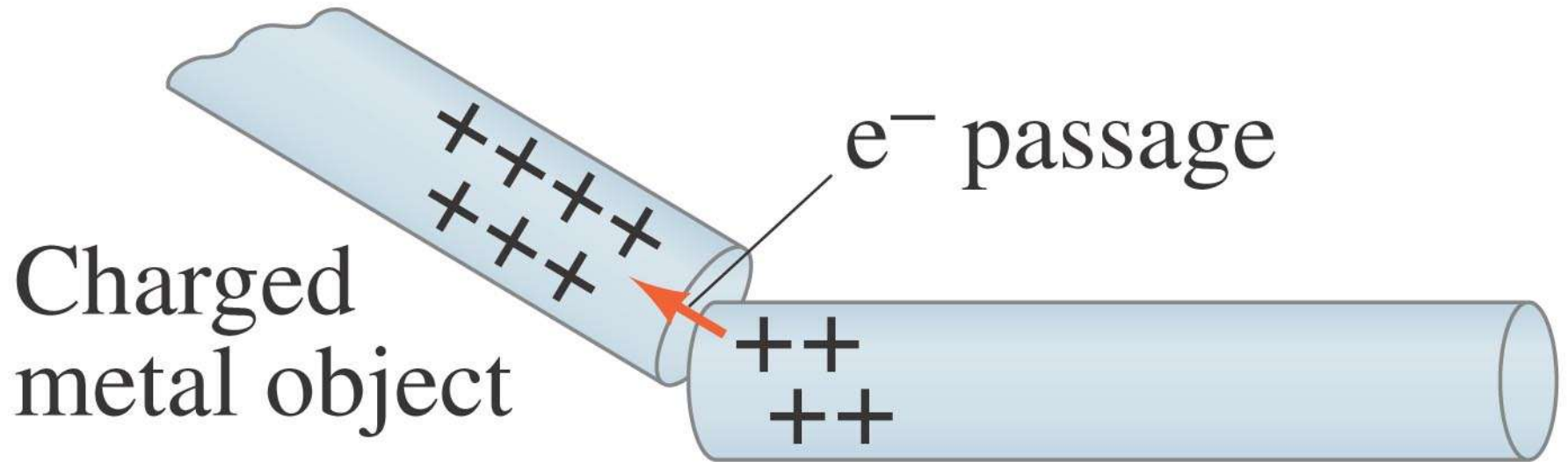


(b) Metal rod acquires charge by contact

(a)



Neutral metal rod

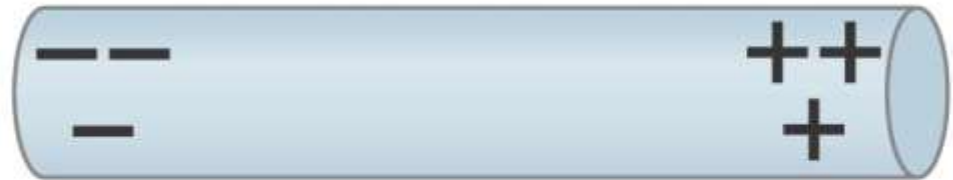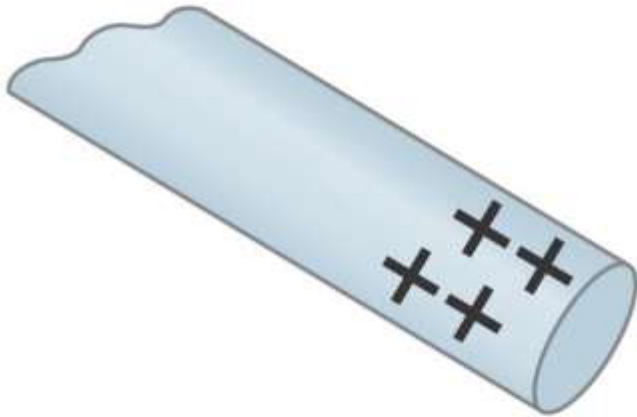

(b)

Metal rod still neutral, but with a separation of charge



Figure 21.8



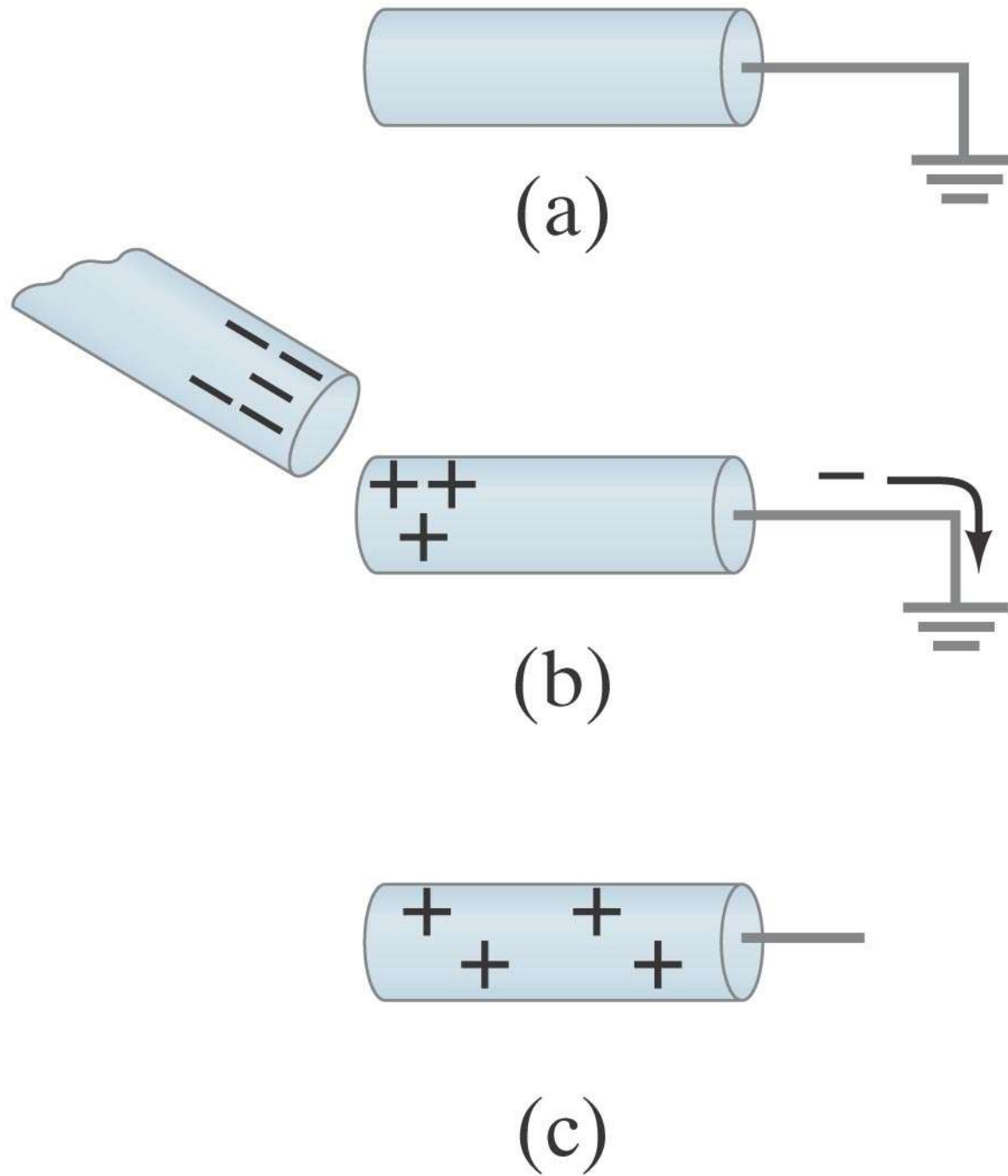
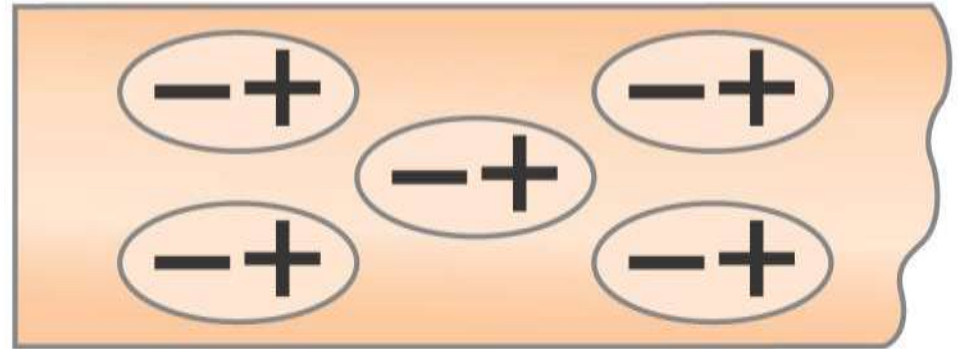


Figure 21.9

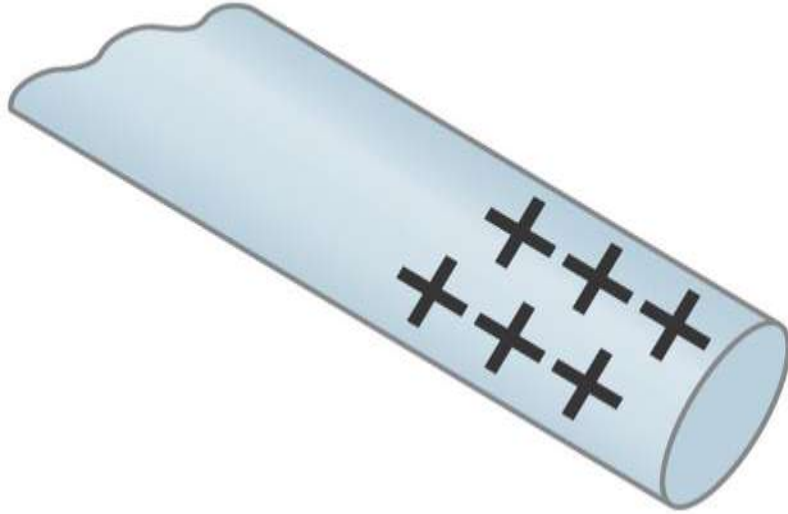


**Nonconductor**

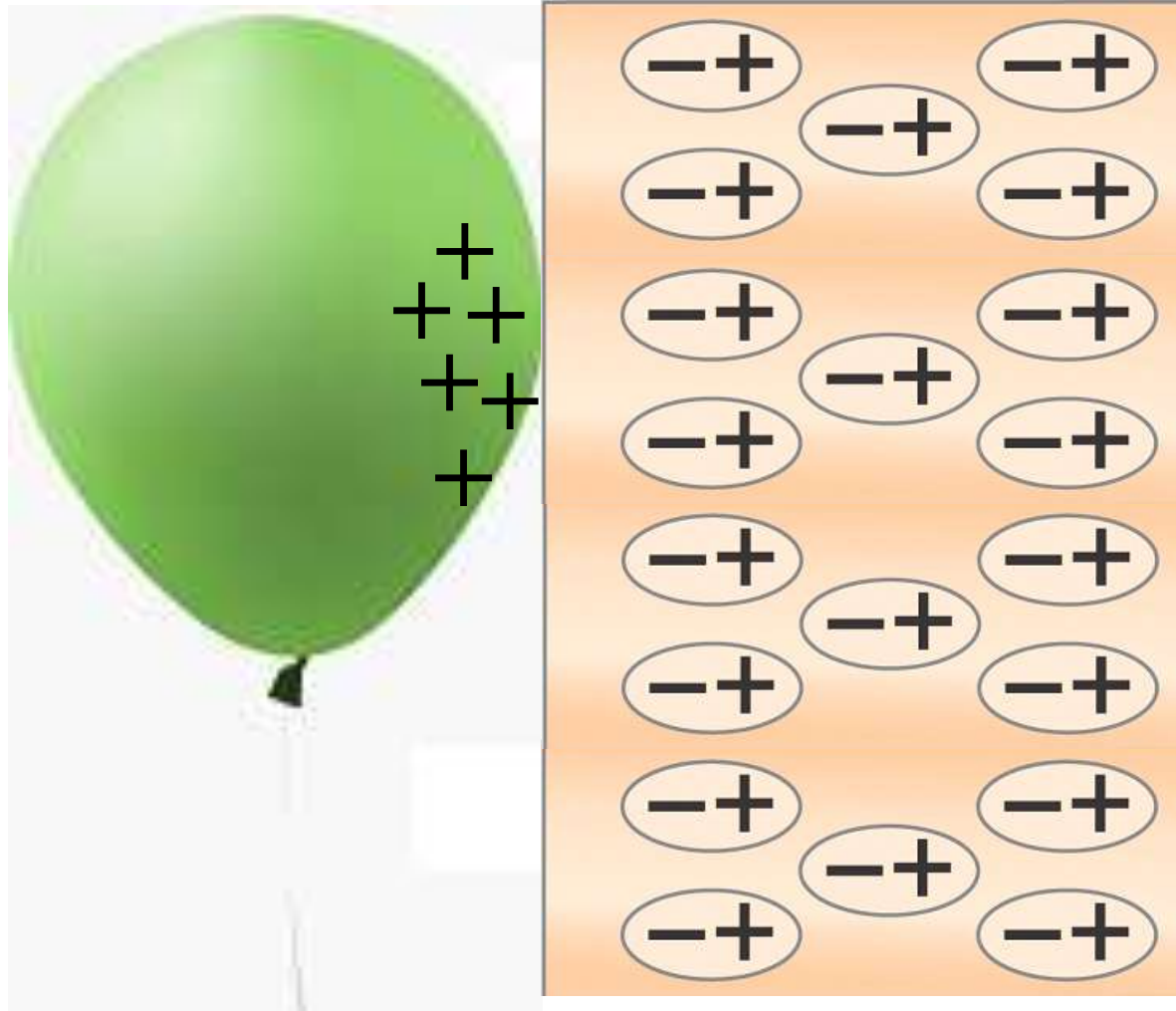


**Surface of wall**

# Charge and Energy

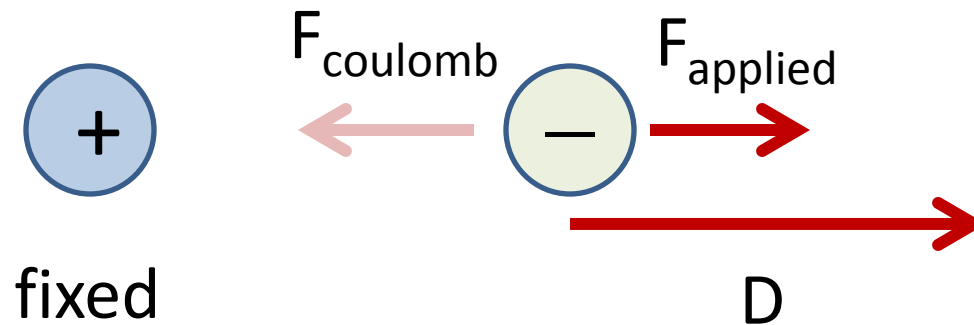

- It takes energy to separate a + & – charge (must do work!)
- Note  $W \neq F_{\text{applied}} D$  since  $F$  varies with position

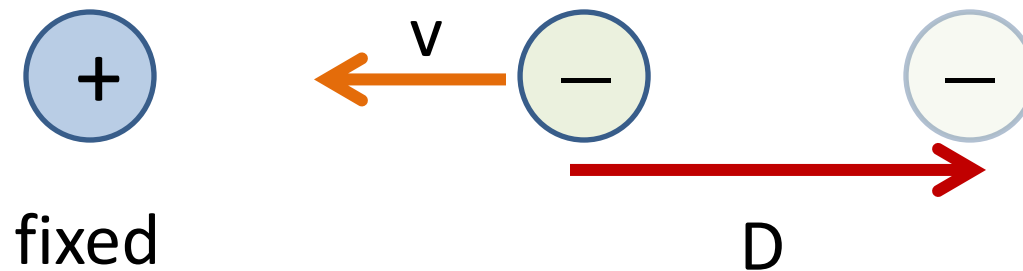- If I release – charge, it moves to + charge



- We say electrostatic potential energy is converted to kinetic energy.

Separated charge  $\Rightarrow$  Stored Energy

- Separating one valence from an otherwise neutral atom, takes only a small amount of work/energy
- But we usually move billions or more!



$q$




$-q$

- Instead of PE, we use *potential difference* (also called *voltage difference*, or just plain *voltage*)

$$\Delta V = \frac{\textit{Work done in separating charge}}{q}$$
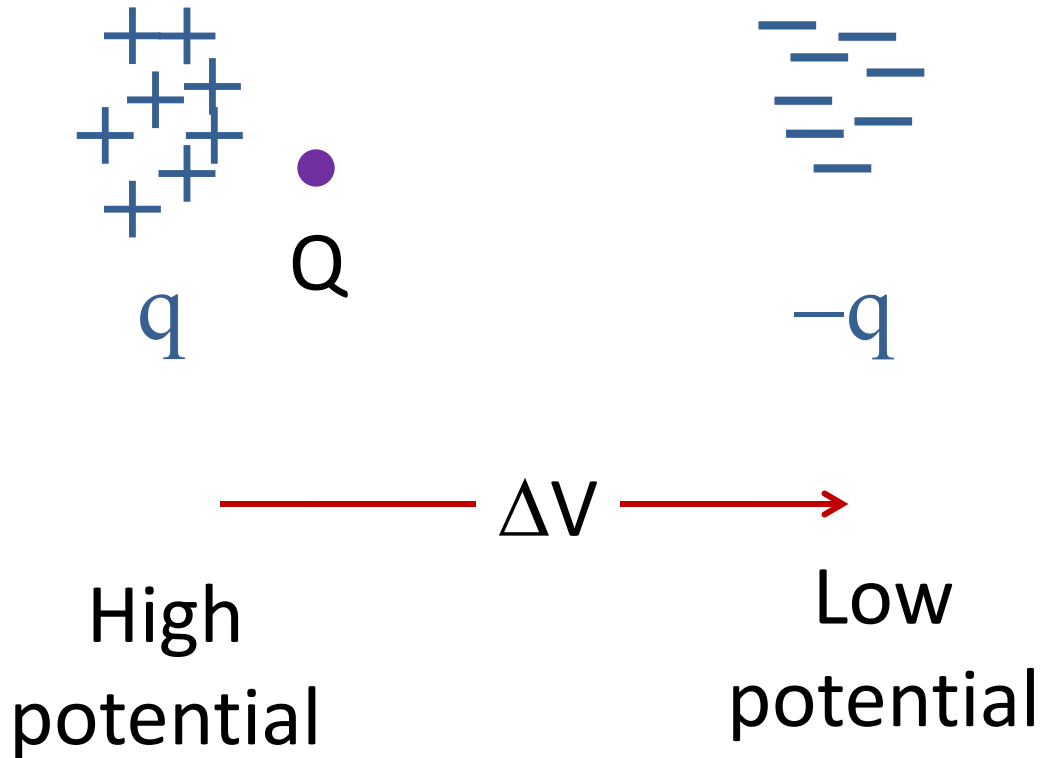
$$= \frac{\textit{Energy of separated charge}}{q}$$




The work done on a small charge  $Q$  by a potential difference  $\Delta V$  is  **$W = Q\Delta V$**



[Questions](#)


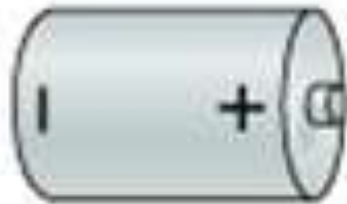
# DC Circuits


- We have two common ways to create/store a charge difference: batteries and capacitors.
- Charge stays in place b/c air is an insulator (usually!).  
If you put provide a conducting path from one side to other, charge will flow (have a current).



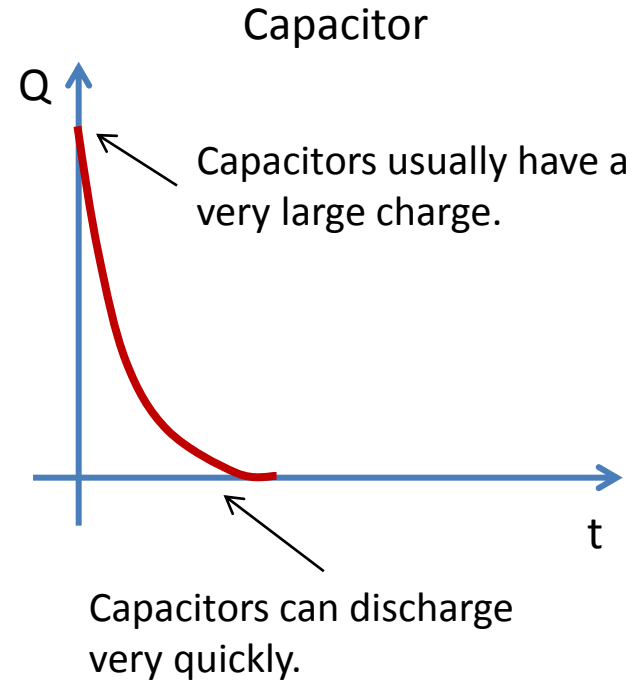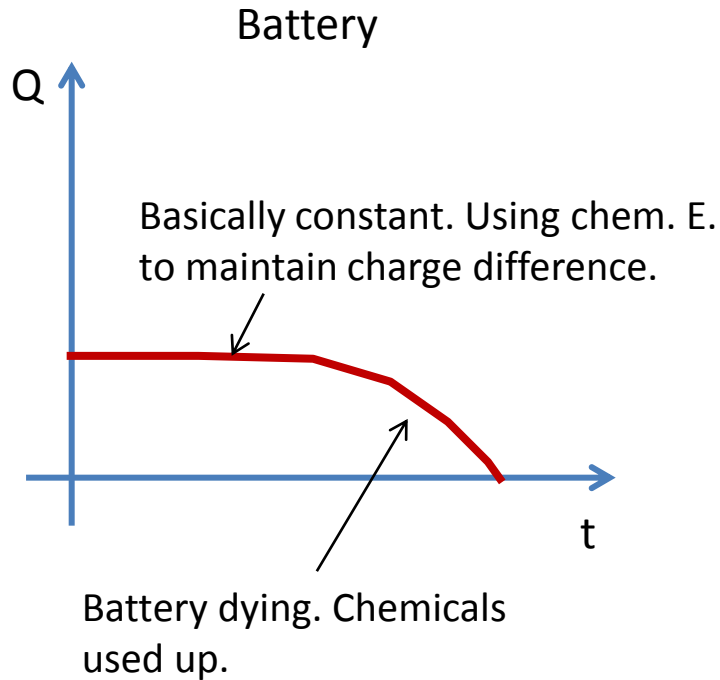



- For an ideal battery we assume a constant  $\Delta V$

# Controlling Current Size - Resistance

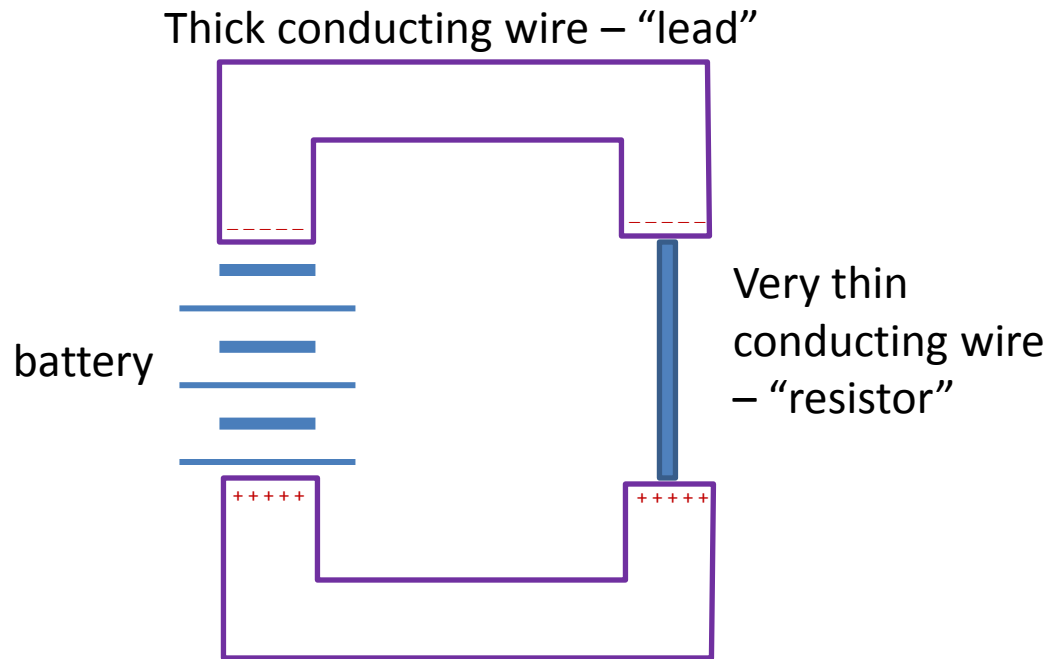


- Resistor “chokes” current
- Charge difference and  $\therefore \Delta V$  across resistor
- $I = \Delta q / \Delta t$  (1 Amp = 1 C/s)
- Electron (negative) current or conventional (positive) current

- Resistance is defined  $R = \Delta V / I$  or  $\Delta V = I R$  (Ohm's Law). Note  $1 \Omega = 1 \text{ V} / \text{A}$
- Plot  $\Delta V$  vs  $I$ . If linear have resistor.
- Resistance dissipates electron KE as heat (collisions between electron and atoms in metal transfer KE to atoms) – Joule Heating  $\leftarrow L \rightarrow$
- $R = \rho L / A$
- Resistivity  $\rho$  is a characteristic of a conductor
- Bulky plastic or ceramic wrapping helps dissipate heat to air without melting resistor

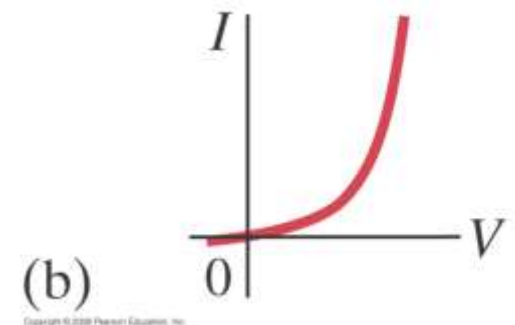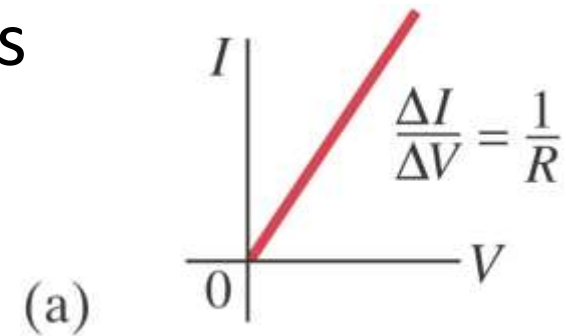
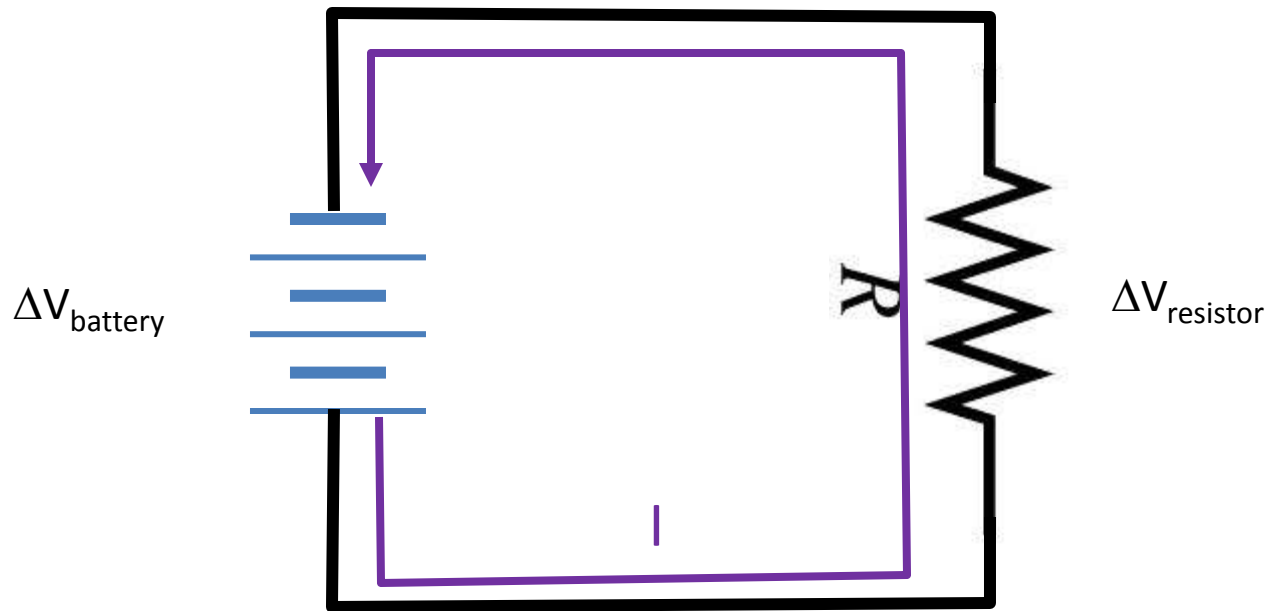
# Energy and Circuits

- Power = Energy / time (1 watt = 1 J /s)
- $P = (\Delta q \Delta V) / \Delta t = \Delta V (\Delta q / \Delta t) = \Delta V I$
- Two ideas and Ohm's Law let's us understand any circuit
- Conservation of Charge
  - Current out of a battery must come back (electrons don't disappear)
- Conservation of Energy
  - Power supplied by batteries in must equal power dissipated by resistors




$$P_{\text{in}} = P_{\text{out}}$$

$$\Delta V_{\text{battery}} \times I = \Delta V_{\text{resistor}} \times I$$

$$\Delta V_{\text{battery}} = \Delta V_{\text{resistor}}$$
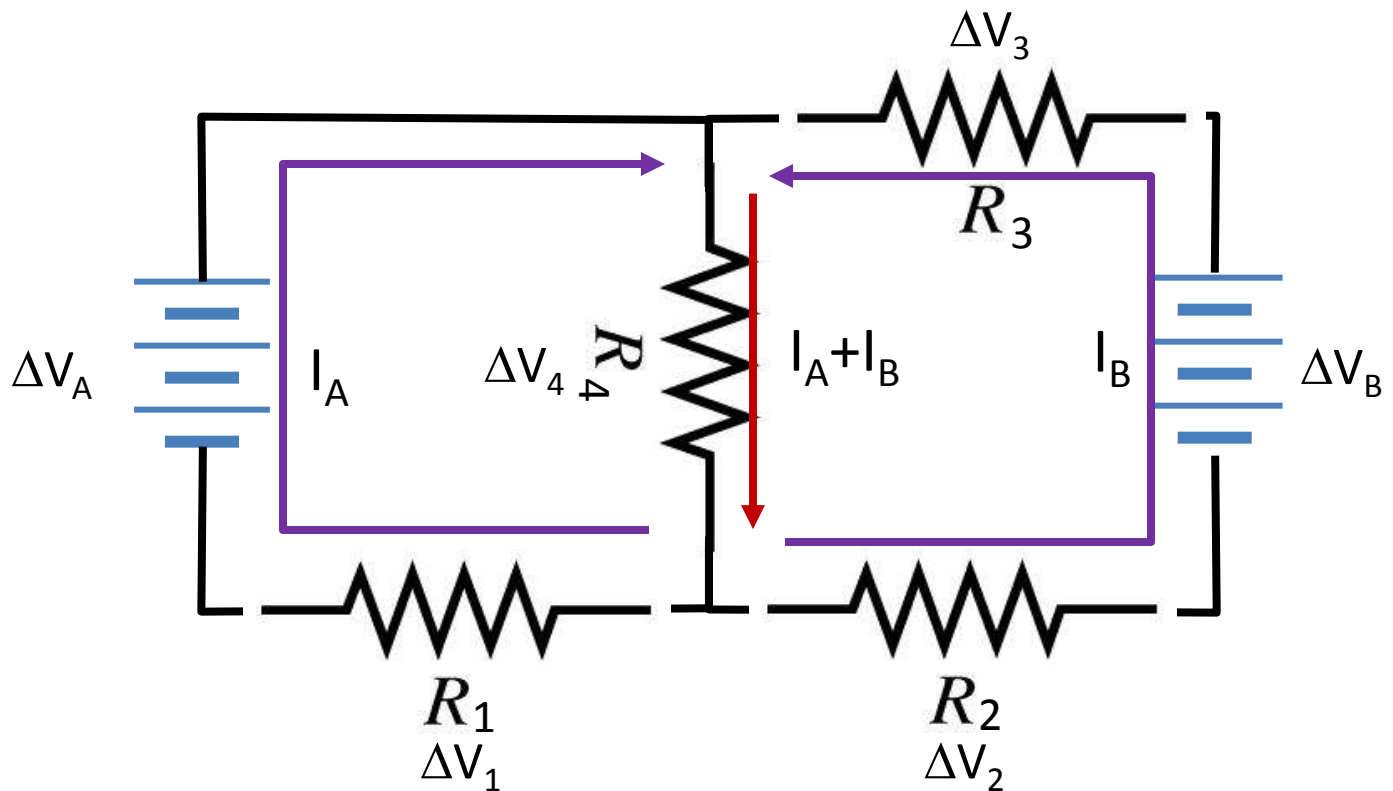
$$\text{Ohm's Law: } I = \Delta V_{\text{battery}} / R$$



$$P_A + P_B - P_1 - P_2 - P_3 - P_4 = 0$$


$$I_A \Delta V_A + I_B \Delta V_B - I_A \Delta V_1 - I_B \Delta V_2 - I_B \Delta V_3 - (I_A + I_B) \Delta V_4 = 0$$

$$I_A (\Delta V_A - \Delta V_1 - \Delta V_4) + I_B (\Delta V_B - \Delta V_2 - \Delta V_3 - \Delta V_4) = 0$$


$$\Delta V_A - \Delta V_1 - \Delta V_4 = 0 \quad \& \quad \Delta V_B - \Delta V_2 - \Delta V_3 - \Delta V_4 = 0$$

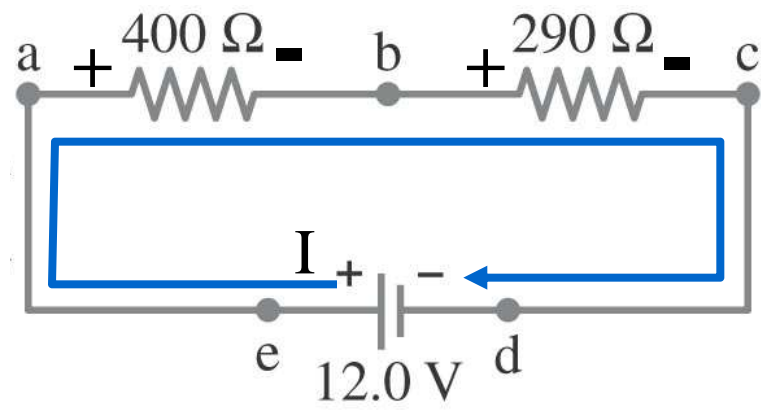KR1: Sum of voltage drops around a loop is zero.






(a)

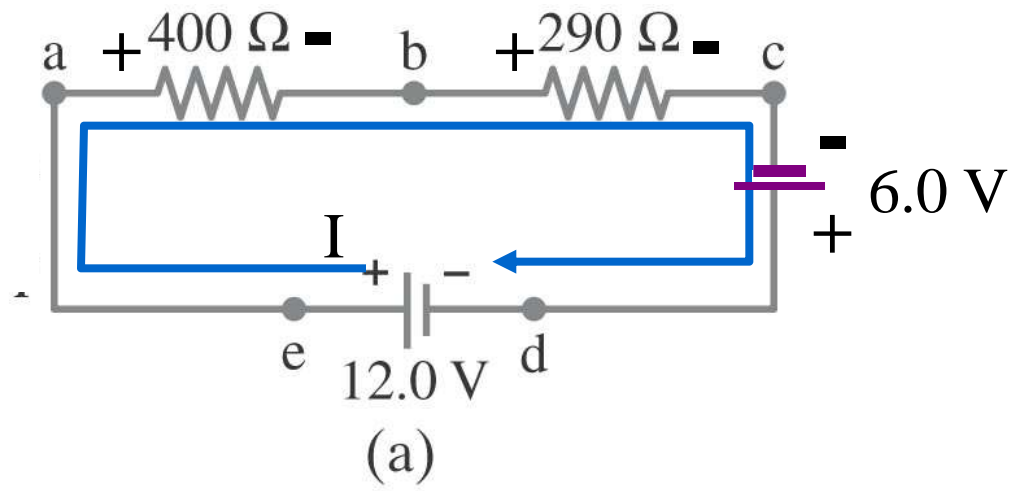
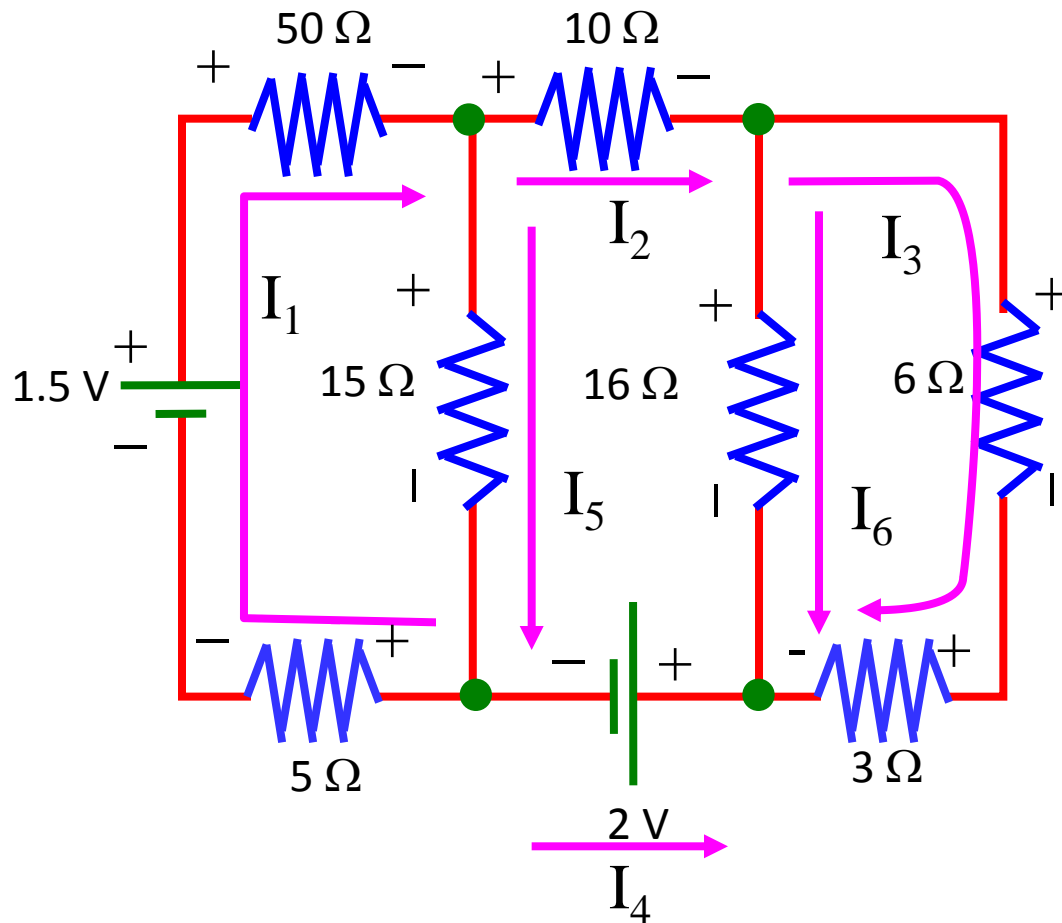
# Using Kirchhoff's Rules

- We use conventional (+) current
- Node/Junction: 3 or more wires join
- Branch: Path from one node to next
  - Assume one current and direction per branch
  - Current flows from high (+) to low (-)
  - $\Delta V = -IR$  if go in direction of current
  - $\Delta V = +IR$  if go opposite to current
- Sum of  $\Delta V$ 's around loop = 0 (KR1)
- Current into node = current out (KR2)



$$1.5 - 50I_1 - 15I_5 - 5I_1 = 0$$


$$I_1 = I_2 + I_5$$

$$2 + 16I_6 + 10I_2 - 15I_5 = 0$$


$$I_2 = I_3 + I_6$$

$$-6I_3 - 3I_3 + 16I_6 = 0$$

$$I_6 + I_3 + I_4 = 0$$

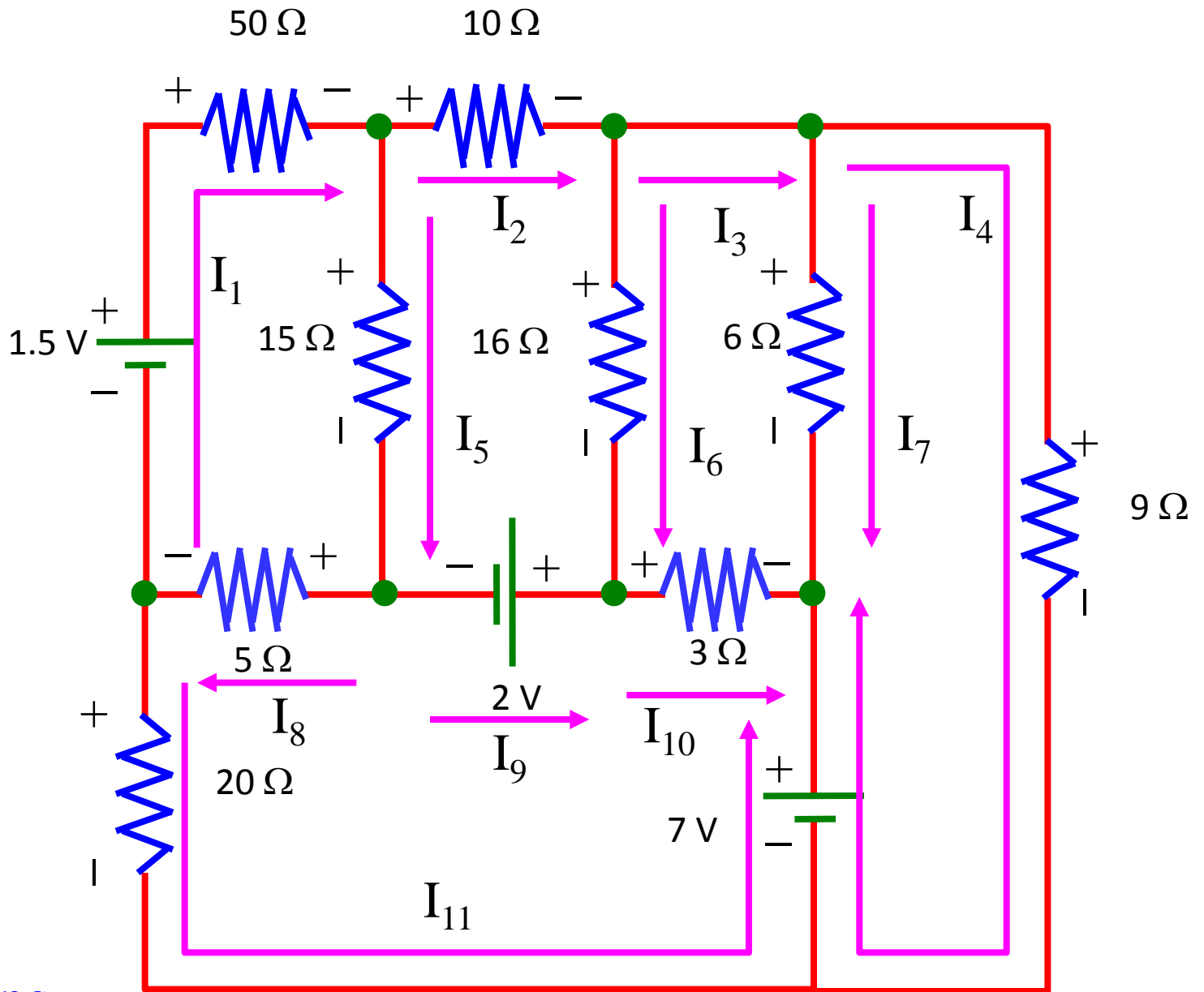


Questions

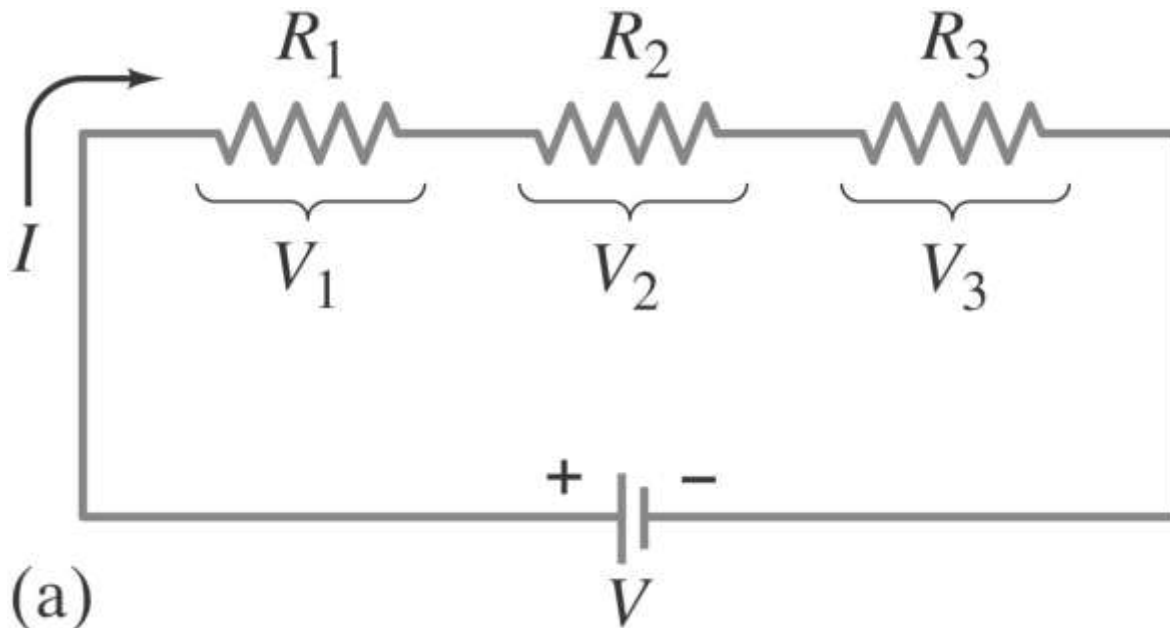

(a)


Copyright © 2008 Pearson Education, Inc.

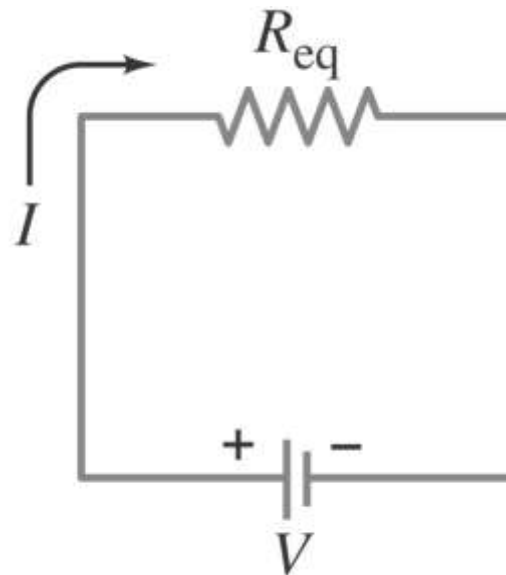

(c)

Copyright © 2008 Pearson Education, Inc.

Equivalent  
Series  
Resistor


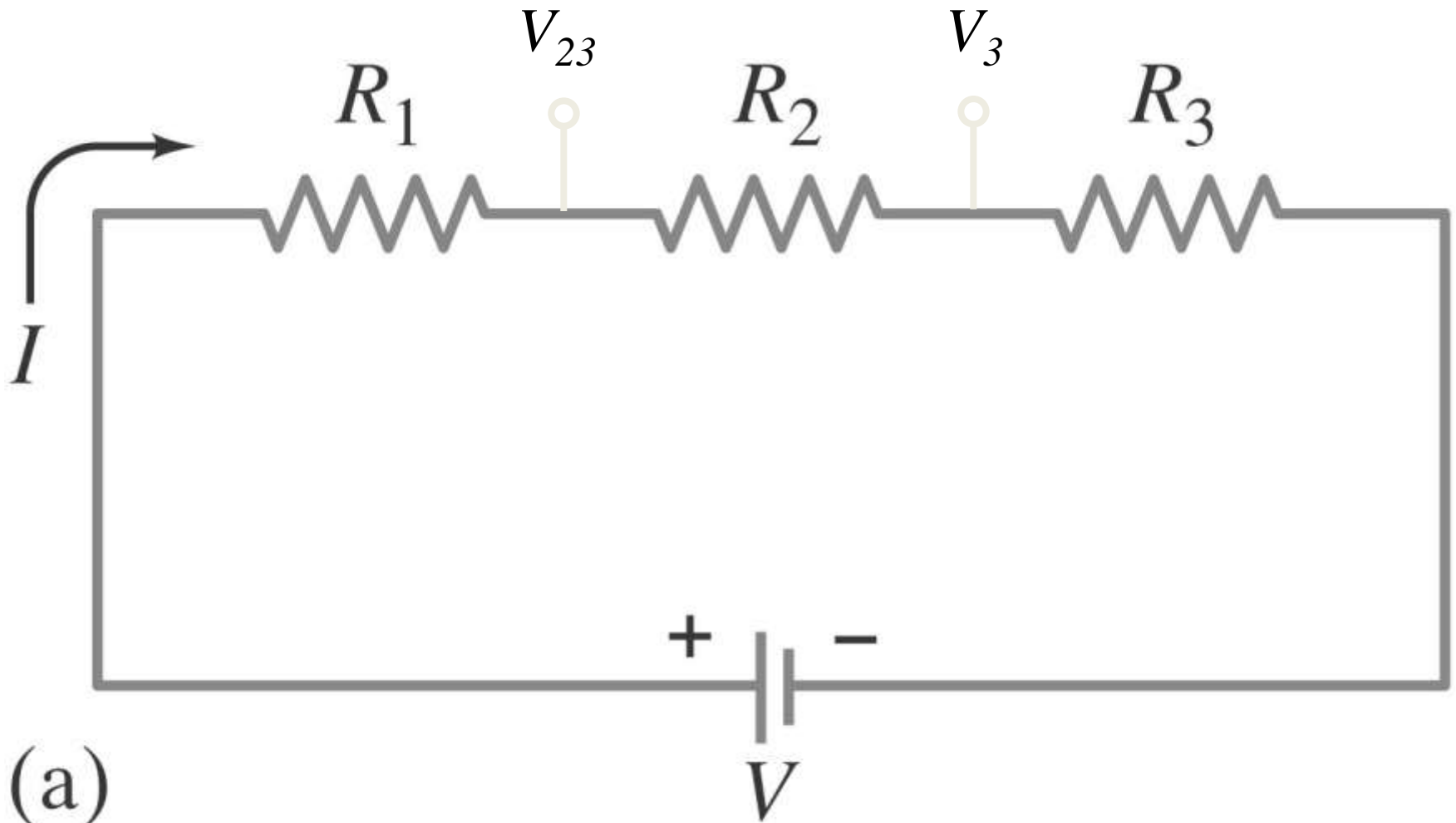


(a)

Copyright © 2008 Pearson Education, Inc.

## Voltage Divider

# Equivalent Parallel Resistor

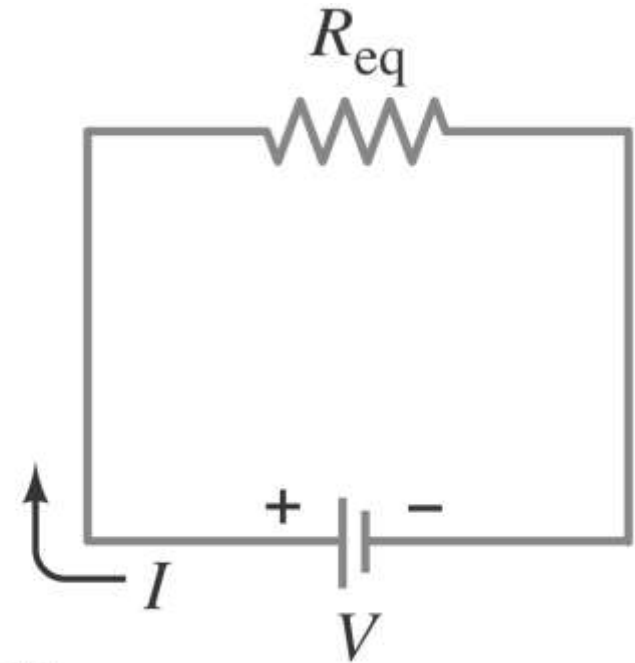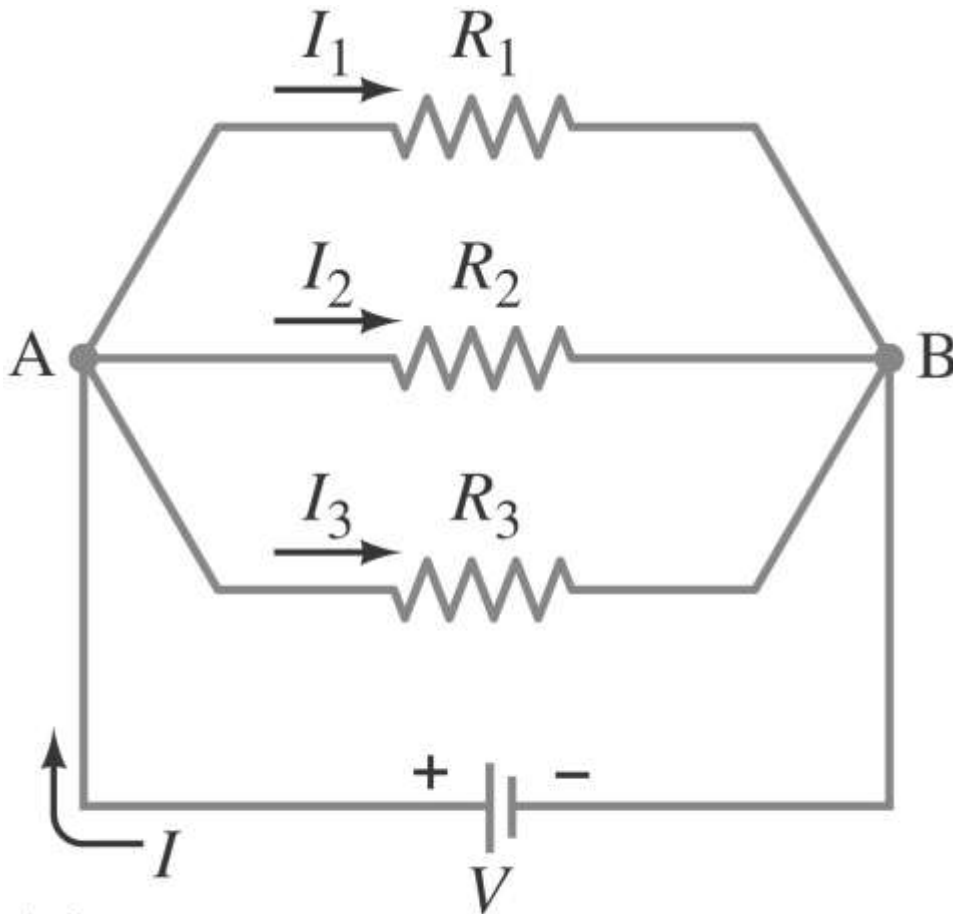

© 2008 Pearson Education, Inc.

(a)


Copyright © 2008 Pearson Education, Inc.



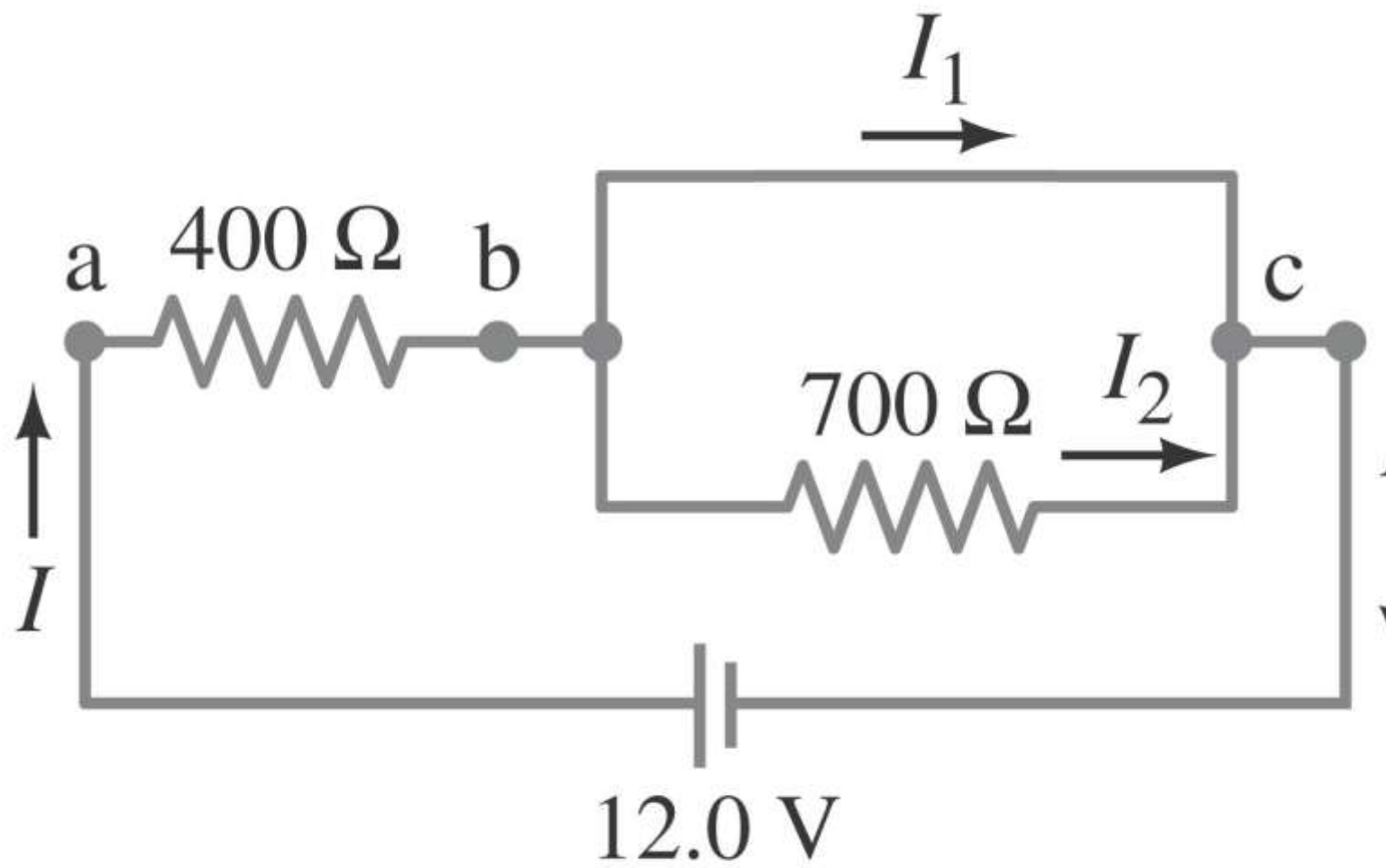
# Short Circuit

A resistor(s) in a branch is shorted if you can go from one node/junction on one side to the other side by a route that has no resistors or batteries.

No current flows through the shorted resistor.




(a)

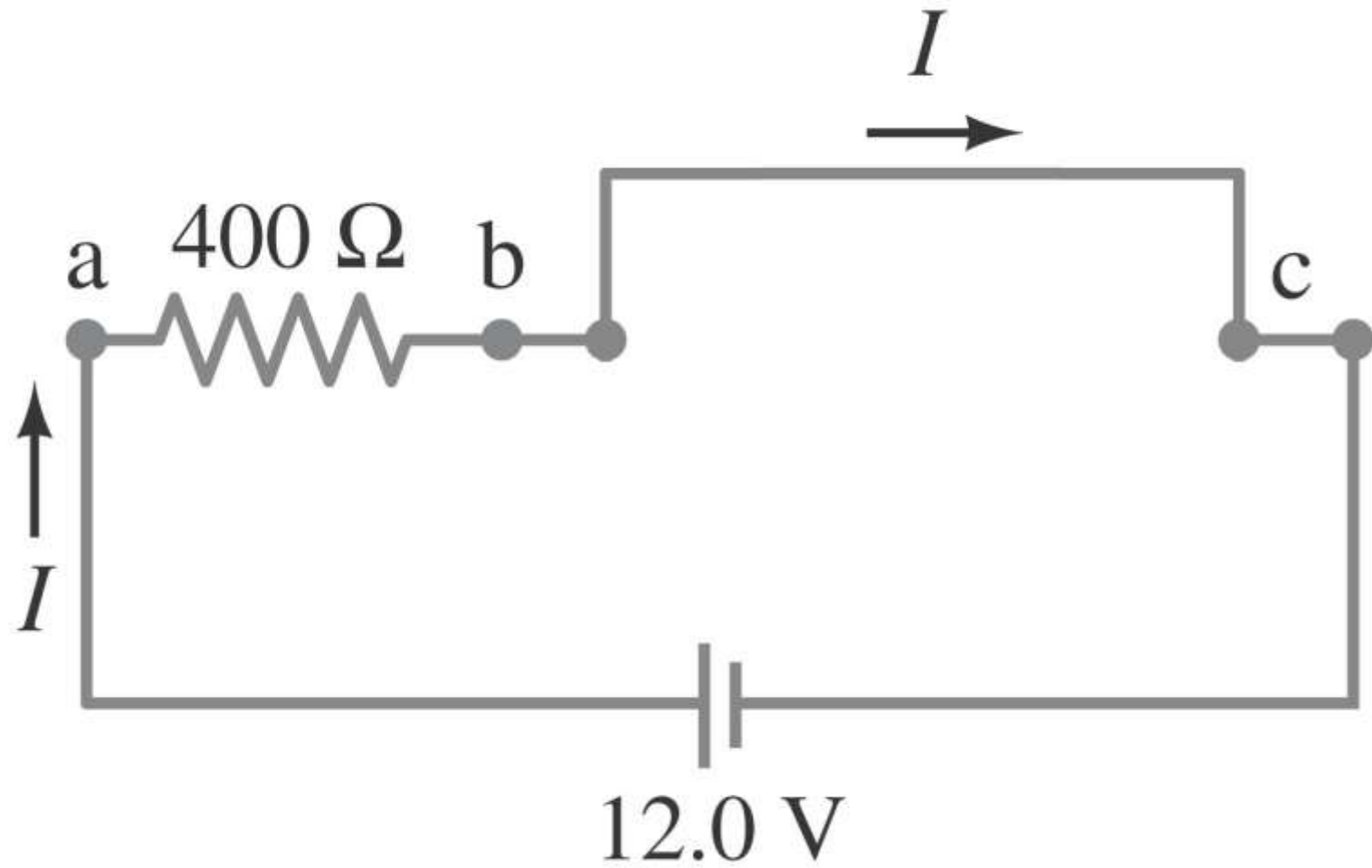


(a)

[Questions](#)

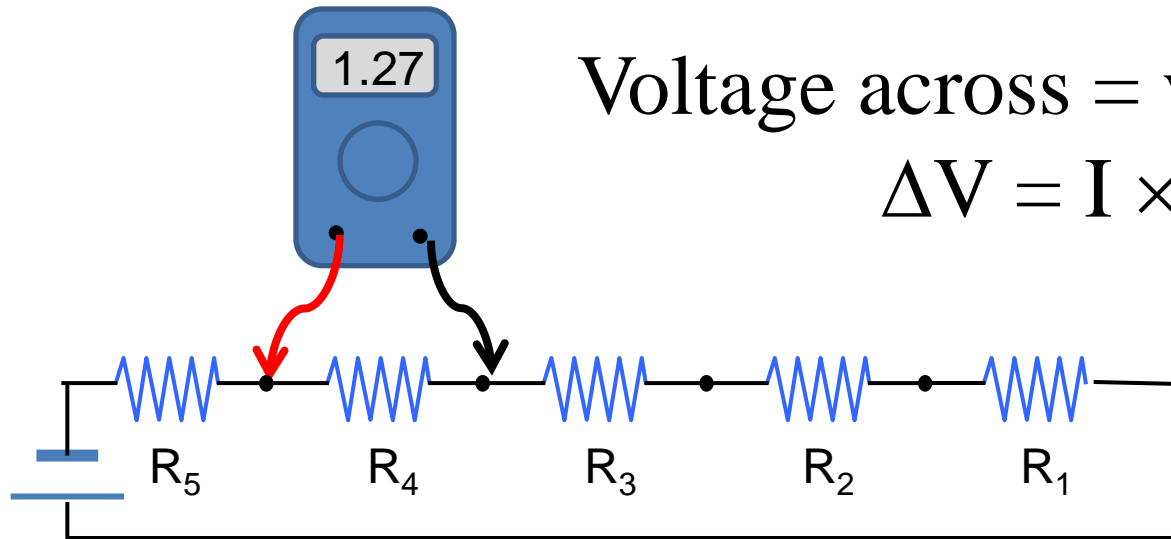

Voltage across = voltage drop


$$\Delta V = I \times R_4$$

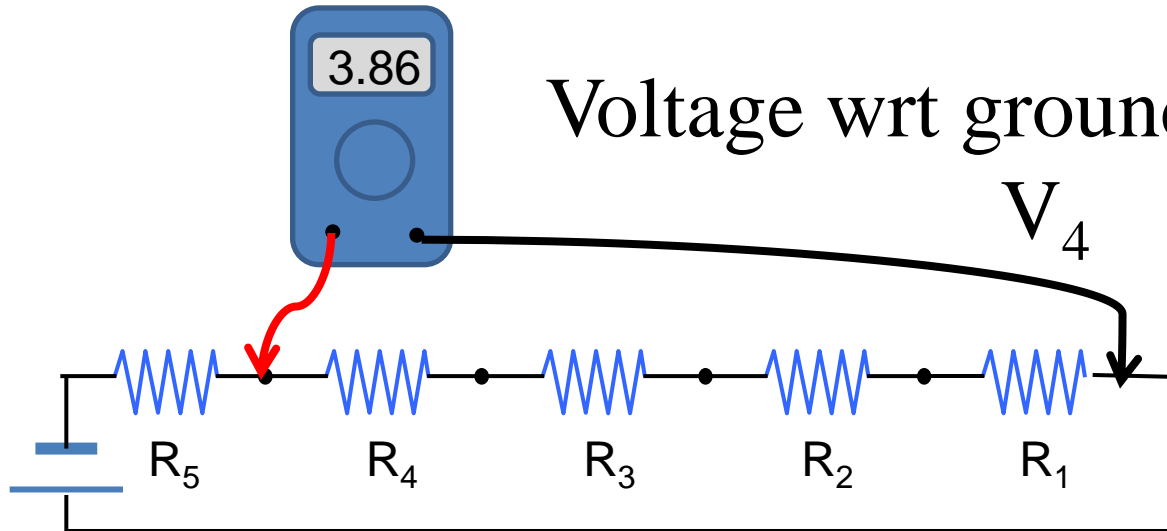

Voltage wrt ground = voltage


$$V_4$$

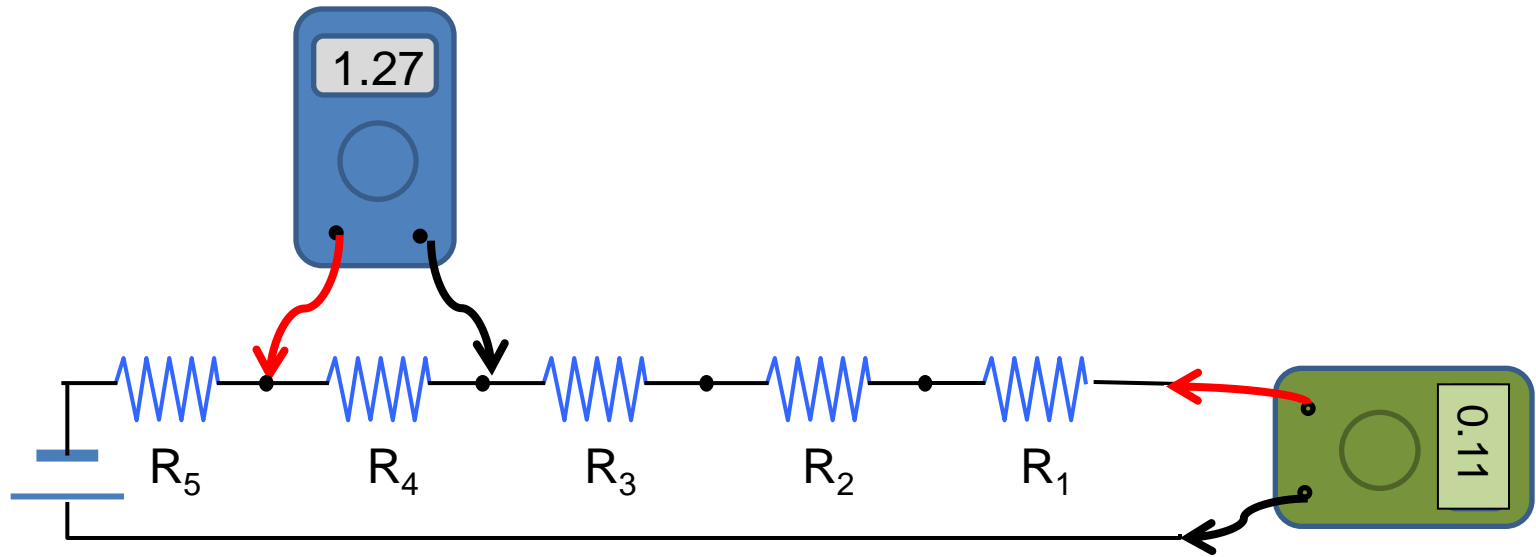One point, often the – side of a battery, is taken as reference or ground or 0 Volts.



- Voltmeters connect in parallel
- $R_{\text{voltmeter}}$  must be  $\gg R_4$  for accurate reading
- Ammeters connect in series
- $R_{\text{ammeter}}$  must be  $\ll R_5 + \dots + R_1$  for accurate reading.

# “Real” Battery

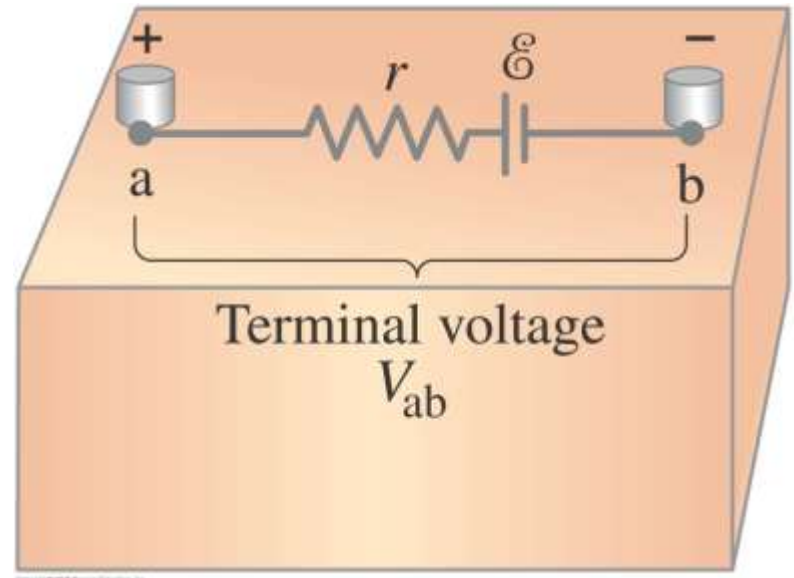

- $\Delta V_{\text{battery}} = \mathcal{E} - I r$
- EMF  $\mathcal{E}$  is fixed
- $r$  increases as battery dies
- Voltmeter cannot tell you if battery dead ( $I \cong 0$  since  $R_{\text{voltmeter}}$  is huge, voltmeter only reads  $\mathcal{E}$ )